

UNIT-1

Transient Analysis

When a network is switched from one condition to another by change in applied voltage or by change in one of the circuit elements during the period of time, branch currents and voltages can change from previous values to new values. This time intervals is called transition Period the response of output of the circuit During transition Period is called Transient Response

A network in which branch currents and node voltages are not changing with respect to time is said to be steady state

Initial conditions:

Let us consider an n^{th} order differential eqn

$$a_0 \frac{d^n i}{dt^n} + a_1 \frac{d^{n-1} i}{dt^{n-1}} + \dots + a_{n-1} \frac{di}{dt} + a_n i = v(t) \quad (1)$$

Initial conditions of the element in the network must be calculated to evaluate arbitrary constants in general form of differential eqns

where

$a_0, a_1, a_2, \dots, a_{n-1}, a_n$ are the constants

$i(t)$ is dependent variable w.r.t circuit

$v(t)$ is independent variable w.r.t circuit

$v(t)$ is a voltage called input or forcing function or excitation

The solution of above equation is known as response of the system

Ex

If we applying Kirchhoff's laws to the network containing energy storing elements like inductor and capacitors and energy dissipating elements like resistor, results in a differential equation to solutions consists of two parts they are complementary function and Particular solution

- * Complementary function represents transient response which decays w.r.t to time.
- * Particular solution represents steady state part of the solution.

$$a_0 \frac{di}{dt} + a_1 i(t) = v(t)$$

The above equation can be classified into two ways

$$a_0 \frac{di(t)}{dt} + a_1 i(t) = v(t)$$

* Homogeneous equation

* Non-Homogeneous equation

Homogeneous equation having zero(0) response

Now $a_0 \frac{di(t)}{dt} + a_1 i(t) = 0$ — Homogeneous

Non-Homogeneous equation is a linear equation which involves in the function $v(t)$

Now $a_0 \frac{di(t)}{dt} + a_1 i(t) = v(t)$ — Non-Homogeneous

Solution of Homogeneous equation:

Finding Solution means to get the expression of $i(t)$

$$a_0 \cdot \frac{di(t)}{dt} = -a_1 i(t)$$

$$a_0 \cdot \frac{di(t)}{i(t)} = -a_1 dt$$

$$\frac{di(t)}{i(t)} = -\frac{a_1}{a_0} dt$$

Integration on b.s

$$\int \frac{di(t)}{i(t)} = \int -\frac{a_1}{a_0} dt$$

$$\int \frac{1}{i(t)} di(t) = -\frac{a_1}{a_0} \int dt + K$$

$$\log i = -\frac{a_1}{a_0} t + K$$

where 'K' is the Integration constant

Take log on b.s

$$\log i = \log \left(\frac{-a_1}{a_0} t + K \right)$$

$$\log i = \log [e^{-a_1/a_0 t}] + \log K$$

$$\log i = \log [e^{\frac{a_1}{a_0} t} K]$$

If integration constant is unknown then the solution is general solution

If some initial information is provided about the network for which constant of integration is evolved then the solution is called as particular solution

Ex: ~~assume two buses had voltage A~~

If we know that at $t=0$ the value of $i(t)$ is a_2 in particular solution

- * For higher order differential equation the no. of arbitrary constants are equal to order of the equation.
- * If this unknowns are to be evaluated for the particular solution of, conditions must be known.
- * Let us assume that reference time $t=0$, network condition is changed by switching action. Assume that switches open at zero time network condition at this instant called initial condition of network.
- * To distinguish the time just before and just immediately after the condition they will use negative and positive signs this $t(0^-)$ and $t(0^+)$


where $t(0^-)$ is instant at which the condition of the network is not at change but it is above to the change

$t(0^+)$ is the instant at which the condition of the network is just changed

Initial conditions of the network depends upon past condition before instant ($t=0^-$). This conditions are at $t=0^-$ are given by voltage across the capacitor and current to the inductor. This are very important value because after switching ($t=0^+$) new currents and voltages are appeared in the network.

Initial conditions of Ideal Elements

Resistor:

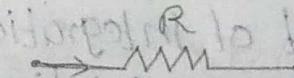


A Resistor both current and voltages are proportional to each other and they are linear relationship and also both are independent of time.

Hence, Resistor allows instantaneous change of currents and voltages

$$V = IR \Rightarrow I = \frac{V}{R}$$

$$T \downarrow V \propto I \downarrow T$$

Inductor:

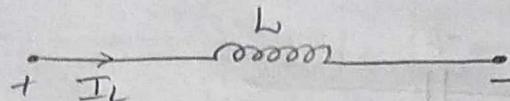

The voltage equation of inductor is given by

$$V_L = L \cdot \frac{di_L}{dt}$$

If DC current through the inductor $\frac{di_L}{dt} = 0$. As DC current is constant w.r.t. time hence voltage across the inductor $V_L = 0$. So for the dc quantities are considered in study state inductor acts as short circuit.

Inductor current is given by $I_L = \frac{1}{L} \int v_L dt$

Limits of integration are decided by the previous history that is i.e; $-\infty$ to $t(0^-)$

Let switching takes place at $t=0$. We can split the limits into $-\infty$ to 0^- and 0 to ∞

$$I_L = \frac{1}{L} \int_{-\infty}^t v_L dt$$

$$I_L = \frac{1}{L} \int_{-\infty}^{0^-} v_L dt + \frac{1}{L} \int_{0^+}^t v_L dt$$


In the above equation $\frac{1}{L} \int_{-\infty}^{0^-} v_L dt$ represents previous history of the inductor current: $I_L = i(0^-) + \frac{1}{L} \int_{0^-}^t v_L dt$

At $t = 0^+$ Inductor current can be return as

$$I_L(0^+) = I_L(0^-) - \frac{1}{L} \int_{0^-}^{0^+} v_L dt$$

$I_L(0^-) = I_L(0^+)$ current through the inductor changes instantaneously.
 i.e., current through the inductor before and after is same

Capacitor:

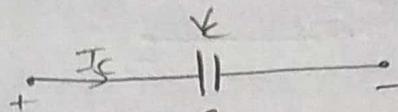

Current through the capacitor is given by $I_C = C \cdot \frac{dV_C}{dt}$.

If dc voltage is applied to capacitor $\frac{dV_C}{dt}$ becomes zero as dc voltage constant w.r.t. time.

Hence current through the capacitor becomes zero.

As far as dc quantities are concerned capacitor acts as open circuit.

Voltage across the capacitor is given $V_C = \frac{1}{C} \int i_C dt$

$$V_C = \frac{1}{C} \int_{-\infty}^t i_C dt$$

The limits can be split into $-\infty$ to 0^- and 0^+ to t

$$V_C = \frac{1}{C} \int_{-\infty}^{0^-} i_C dt + \frac{1}{C} \int_{0^+}^t i_C dt$$













$$V_{C(t)} = V_{C(0^-)} + \frac{1}{C} \int_{0^-}^{0^+} i_C dt$$

$$V_{C(0^+)} = V_{C(0^-)} + 0$$


$$V_{C(0^+)} = V_{C(0^-)}$$

It doesn't allow sudden change

i.e., current through the capacitor before and after switching same.

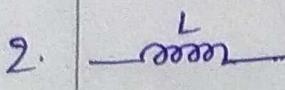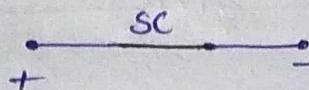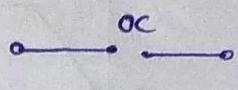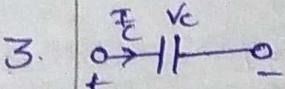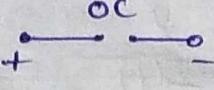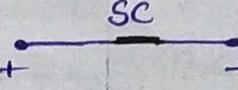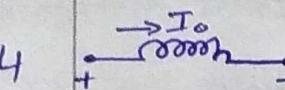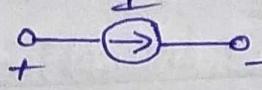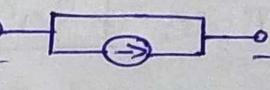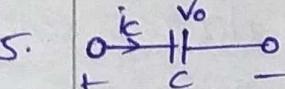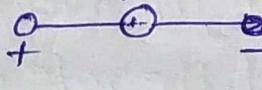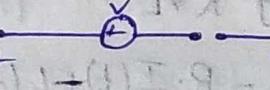
S.No	Element	Behaviour in study state	Behaviour at $t \rightarrow \infty$
1	Resistor	Resistor	Resistor
2.			
3.			
4.			
5.			

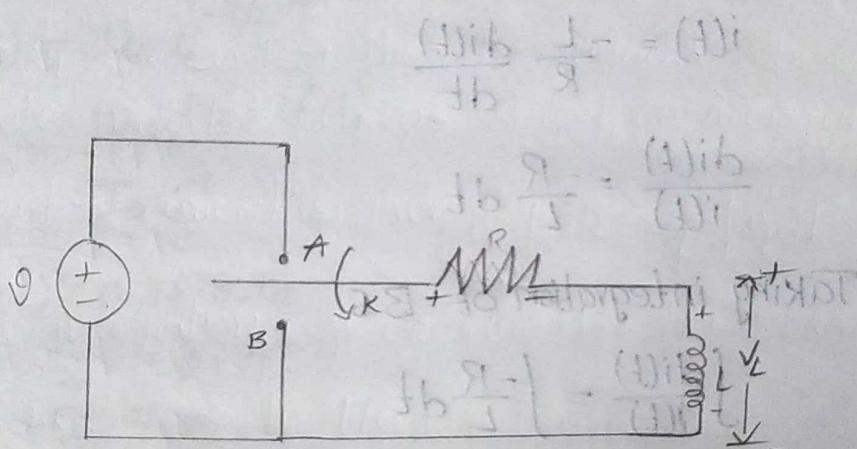Response of source free (or) and reverse series RL circuit:




Consider a series RL circuit. Let switch is kept at position A before $t=0$. Transition network is in study state assume at $t=0$ now switch is move to position B

At $t=0^-$ (at Position A)

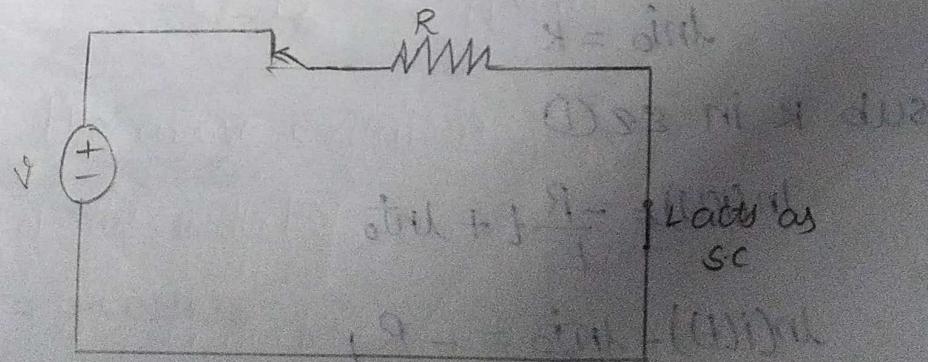

$$I(0^-) = I(0^+) \Rightarrow I_0 \Rightarrow \frac{V}{R}$$

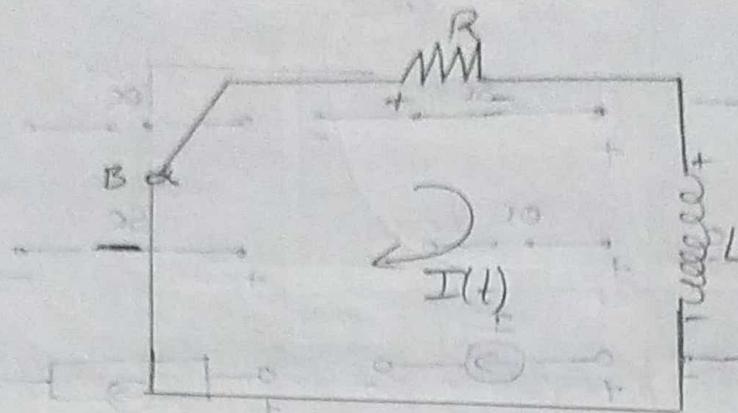Because current to the inductor can not change instantaneously
at $t \geq 0$ at position B



Applying KVL

$$-R \cdot I(t) + L \frac{dI(t)}{dt} = 0$$

$$-L \frac{dI(t)}{dt} = RI(t)$$

$$i(t) = -\frac{L}{R} \frac{dI(t)}{dt}$$

$$\frac{dI(t)}{i(t)} = -\frac{R}{L} dt$$

Taking integration of BS

$$\int \frac{dI(t)}{i(t)} = \int -\frac{R}{L} dt$$

$$\ln(i(t)) = -\frac{R}{L} t + K \quad \text{①}$$

$$i(t) = e^{-Rt/L} e^K$$

Initially condition $t=0$

$$\ln i_0 = -\frac{R}{L} 0 + K$$

$$\ln i_0 = K$$

sub K in eq ①

$$\ln(i(t)) = -\frac{R}{L} t + \ln i_0$$

$$\ln(i(t)) - \ln i_0 = -\frac{R}{L} t$$

$$\ln \frac{i(t)}{I_0} = -\frac{R}{L}t$$

$$i(t) = I_0 e^{-Rt/L}$$

$$i(t) = I_0 e^{-Rt/L} t$$

From the above equation in source we RL series circuit
the current through the inductor is exponentially decreases

let us substitute different values of T as $T, 2T, 4T, 6T$...

where $T \rightarrow$ Time constant

$$T = \frac{1}{R/L}$$

$$(i(t)) = I_0 e^{-R/L \cdot T}$$

$$= I_0 e^{(-R/L) \cdot (1/R)}$$

$$= I_0 e^{-1}$$

$$i(t) = 0.3678 I_0$$

$$t = 2T$$

$$i(t) = I_0 e^{-R/L \cdot 2T}$$

$$= I_0 e^{-R/L \cdot 2(1/R)}$$

$$= I_0 e^{-2}$$

$$i(t) = 0.1353 I_0$$

$$t = 4T$$

$$i(t) = I_0 e^{-R/L \cdot 4T}$$

$$= I_0 e^{-R/L \cdot 4(1/R)}$$


$$= I_0 e^{-4}$$

$$i(t) = 0.0183 I_0$$

$$t = 6T$$

$$i(t) = 0.0024 I_0$$

$$i(t)$$

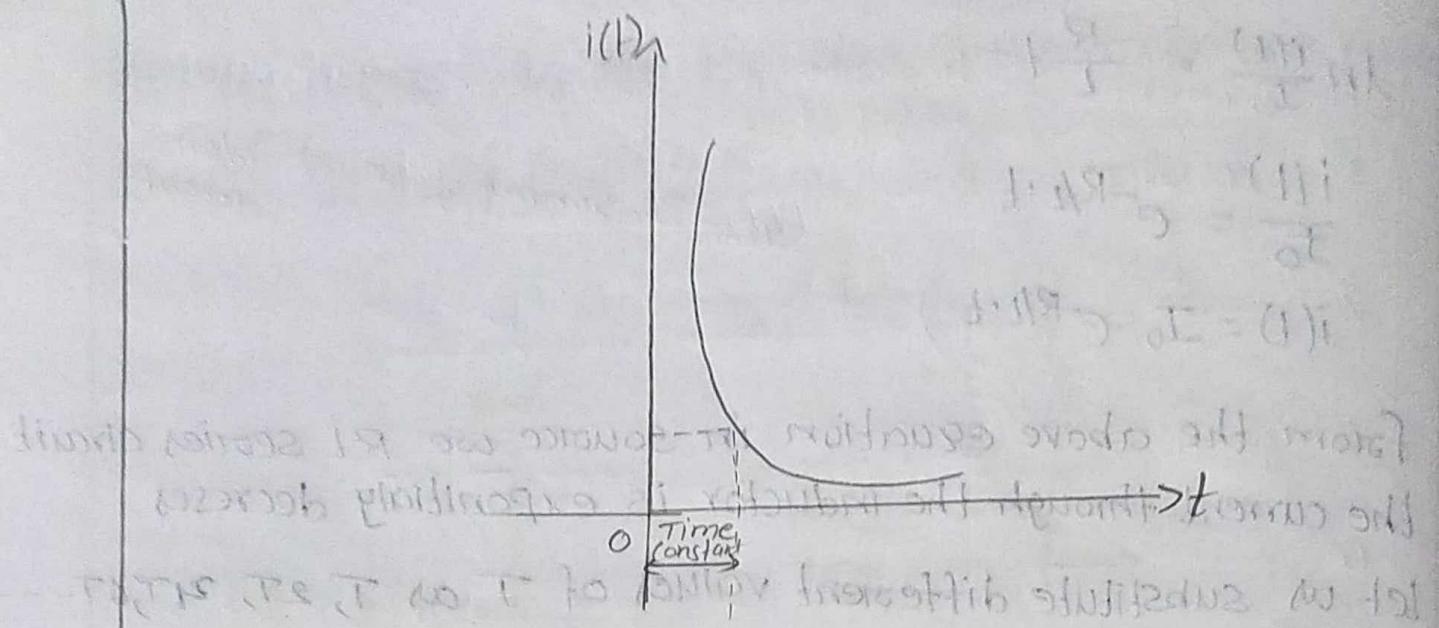

Initial the current through the inductor decreases rapidly to $0.3678 I_0$ times after that the rate of decaying ~~slow~~ down and reaches to steady state and apparently $I =$

Voltage across the inductor is given by $V_L = L \cdot \frac{di(t)}{dt}$

$$V_L = L \cdot \frac{d}{dt} [I_0 e^{-R/L t}]$$

$$i(t) = I_0 e^{-R/L t}$$


$$V_L = L \frac{d}{dt} [I_0 e^{-R/L t}]$$

$$V_L = L \cdot I_0 (-\frac{R}{L}) \cdot e^{-R/L t}$$

$$V_L = -I_0 R \cdot e^{-R/L t}$$

But we known that $V = I_0 R$


$$V_L = V \cdot e^{-R/L \cdot t}$$

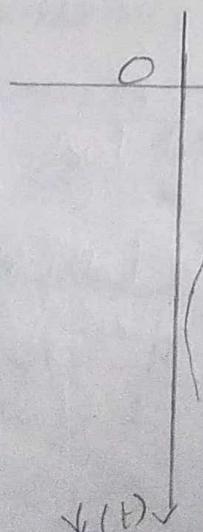


* For physical (or) general interpretation before switch is move to position B the stored energy in the inductor is $\frac{1}{2}LI^2$ and energy dissipated in the resistor is I^2R .

* After source removed energy stored in the inductor is totally dissipated by the resistor.

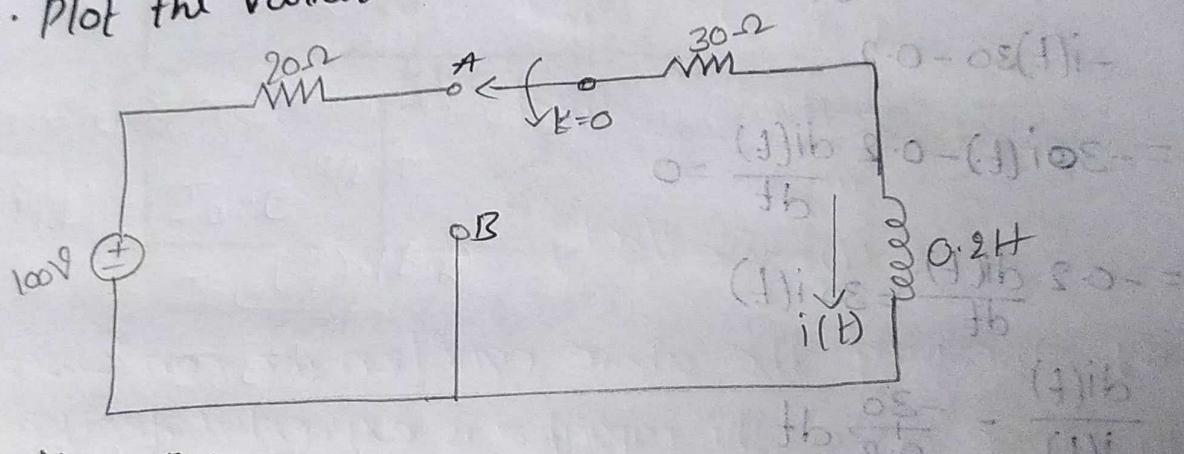The circuit shown in the fig, initially the switch is kept at position A for long time. At $t=0$ switch is moved to position B - find the expression for the current for $t > 0$ find the value of current at $t=6.667\text{ ms}$, the t point 333ms, 20ms. Plot the variation of current through the inductor.



At position B

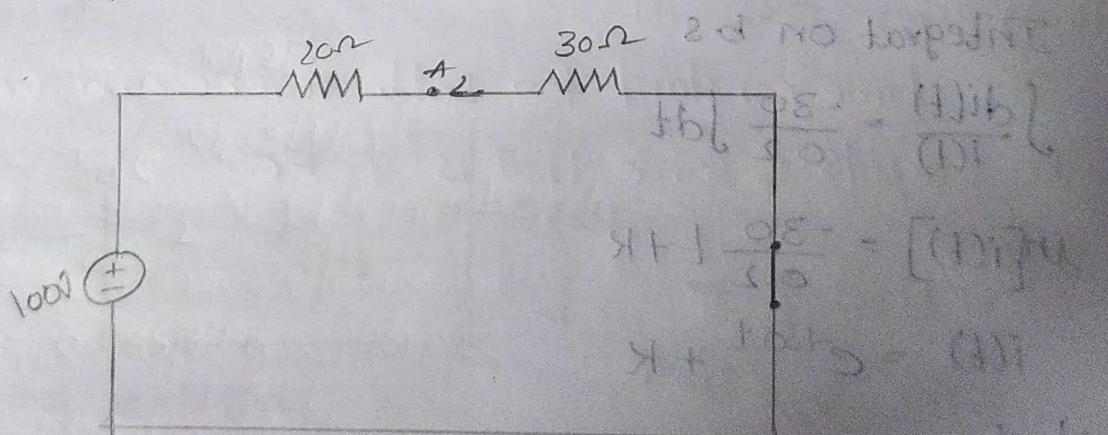


$$t=0^-$$

$$i(0^-) = i(0^+) = I_0 = \frac{V}{R}$$

$$i(0^-) = I_0 = \frac{100}{20+30} = 2\text{ A}$$

At Position B

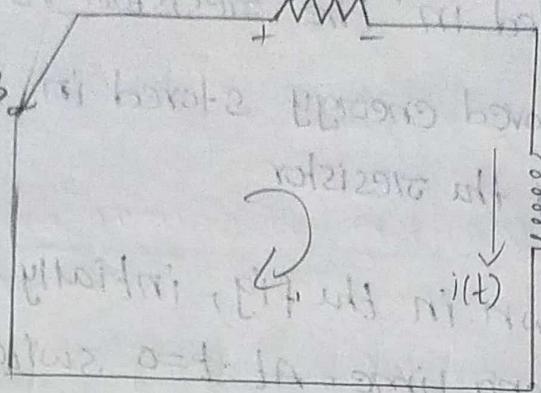

By Applying KVL

$$-i(t) \cdot R - L \cdot \frac{di(t)}{dt} = 0$$

$$-i(t) \cdot 30 - 0.2 \cdot \frac{di(t)}{dt} = 0$$

$$= -30i(t) - 0.2 \frac{di(t)}{dt} = 0$$

$$= -0.2 \frac{di(t)}{dt} = 30i(t)$$

$$\frac{di(t)}{i(t)} = -\frac{30}{0.2} dt$$

Integrate on both sides

$$\int \frac{di(t)}{i(t)} = -\frac{30}{0.2} \int dt$$

$$\ln[i(t)] = -\frac{30}{0.2} t + K$$

$$i(t) = e^{-150t} + K$$

At $t=0$

$$\ln[i(t)] = -150t + \ln(I_0)$$

$$= \ln[i(t)] - \ln[I_0] = -150t$$

$$= \ln[i(t)/I_0] = e^{-150t}$$


$$i(t) = I_0 e^{-150t}$$

at $t = 6.6667$ ms


$$v(6.6667) = \omega e^{-150} \times 6.6667 \times 10^{-3} + 0.07854$$

$$v(12.334) = \omega e^{-150} \times 12.334 \times 10^{-3} - 0.3786$$
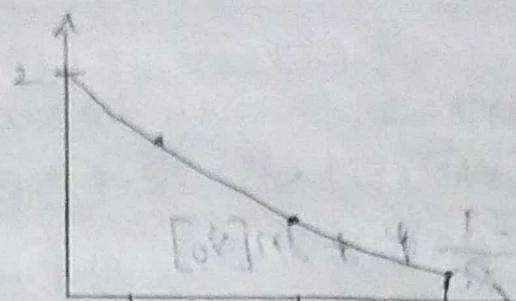
$$i(0) = \omega e^{-150} \times 20 \times 10^{-3} = 0.0953 \text{ A}$$




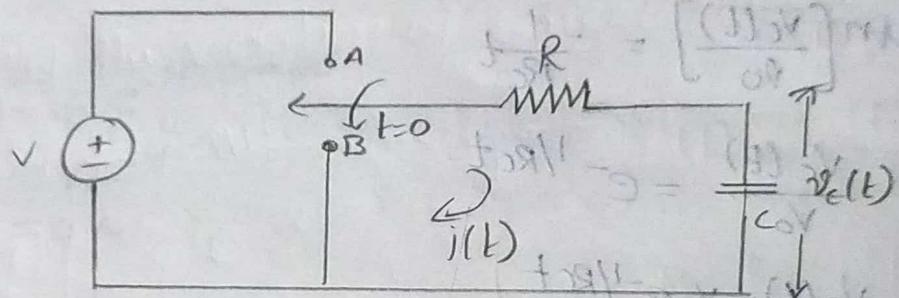Response of source free R-C series circuit:



$$v(0) = V_0 = i(0^+)$$

At Position B

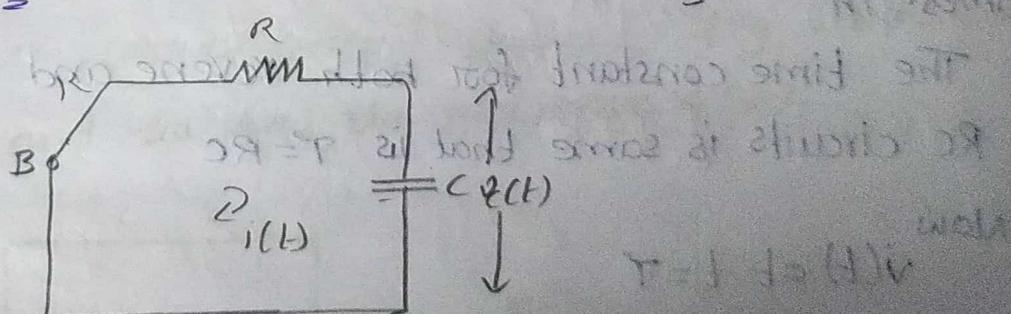

Applying KVL

$$-Ri(t) - v_c(t) = 0$$

$$i(t) = C \frac{dv_c(t)}{dt}$$

$$RC \frac{dv_c(t)}{dt} = -v_c dt$$

$$\frac{dv_c(t)}{v_c(t)} = -\frac{1}{RC} dt$$

Integration on LHS

$$\int \frac{dV_c(t)}{dt} = \frac{1}{RC} - \frac{1}{RC} \int dt$$

$$dV_c(t) \ln[V_c(t)] = -\frac{1}{RC} t + K$$

At $t=0$

$$\ln[V_0] = K$$

$$\ln[V_c(t)] = -\frac{1}{RC} t + \ln[V_0]$$

$$\ln[V_c(t)] - \ln[V_0] = -\frac{1}{RC} t$$

$$\ln\left(\frac{V_c(t)}{V_0}\right) = -\frac{1}{RC} t$$

$$\frac{V_c(t)}{V_0} = e^{-1/RC t}$$

$$V_c(t) = V_0 e^{-1/RC t}$$

By observing the above equation we can observe that the voltage across the capacitor is exponential decayed by V_0 times.

The time constant for both reverse and unreverse series RC circuits is same that is $\tau = RC$

Now

$$V(t) \text{ at } t=\tau$$

$$V_c(t) = V_0 e^{-1/RC \tau}$$

$$= V_0 e^{-1/RC \cdot RC}$$

$$= V_0 e^{-1}$$

$$= 0.367 V_0$$

$$t = 2\tau$$

$$V_c(t) = V_0 e^{-1/RC \cdot 2\tau}$$

$$= V_0 e^{-1/RC \cdot 2RC}$$

$$= V_0 e^{-2}$$

$$= 0.135 V_0$$

$$t = 4T$$

$$V_C(t) = V_0 e^{-1/RC \cdot 4T}$$

$$= V_0 e^{-1/RC \cdot 4RC}$$

$$= V_0 e^{-4}$$

$$= 0.0183 V_0$$

$$t = 6T$$

$$V_C(t) = V_0 e^{-1/RC \cdot 6T}$$

$$= V_0 e^{-1/RC \cdot 6(1/RC)}$$

$$= V_0 e^{-6}$$

$$= 2.478 V_0$$

$$t = \infty$$


$$V_C(t) = V_0 e^{-1/RC \cdot \infty \cdot RC}$$

$$= V_0 e^{-\infty}$$


$$= 0 V_0$$

The voltage across the capacitor reaches to steady state of is equal approximation at $6T$ ($0.0183 V_0$) & $8T$ and becomes zero at ∞

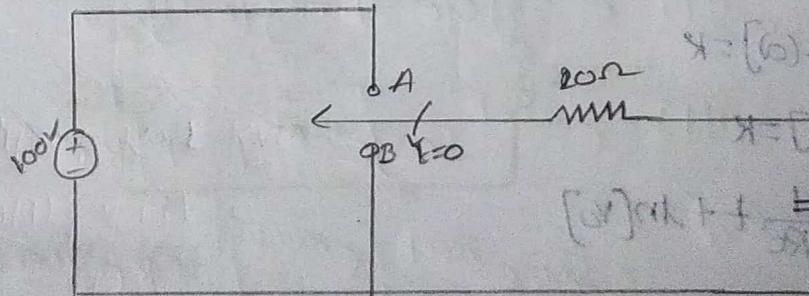~~for a given RC-series circuit shown in fig where $R = 2\text{ ohm}$ and $C = 0.5\text{ F}$ and find the response $V_C(t)$~~




At position A

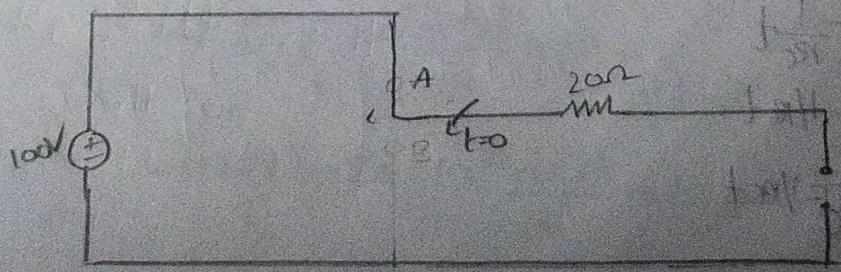

$$V(0^-) = V_0 = V(0^+)$$

At Position B

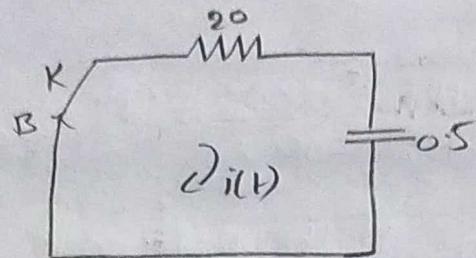

Applying KVL

$$-Ri(t) - V_c(t) = 0$$

$$-RC \frac{dV_c(t)}{dt} = V_c(t)$$

$$\frac{dV_c(t)}{V_c(t)} = -\frac{1}{RC} dt$$

I.O.B.S

$$\int \frac{dV_c(t)}{V_c(t)} = -\frac{1}{RC} \int dt$$

$$\ln[V_c(t)] = -\frac{1}{RC} t + K$$

At $t=0$

$$\ln[V_c(0)] = K$$

$$\ln[V_0] = K$$

$$\ln[V_c(t)] = -\frac{1}{RC} t + \ln[V_0]$$

$$\ln[V_c(t)] - \ln[V_0] = -\frac{1}{RC} t$$


$$\ln[V_c(t)/V_0] = -\frac{1}{RC} t$$

$$V_c(t) = V_0 e^{-1/RC t}$$

$$V_c(t) = 100 e^{-1/RC t}$$

Non-Homogenous (RL circuit)

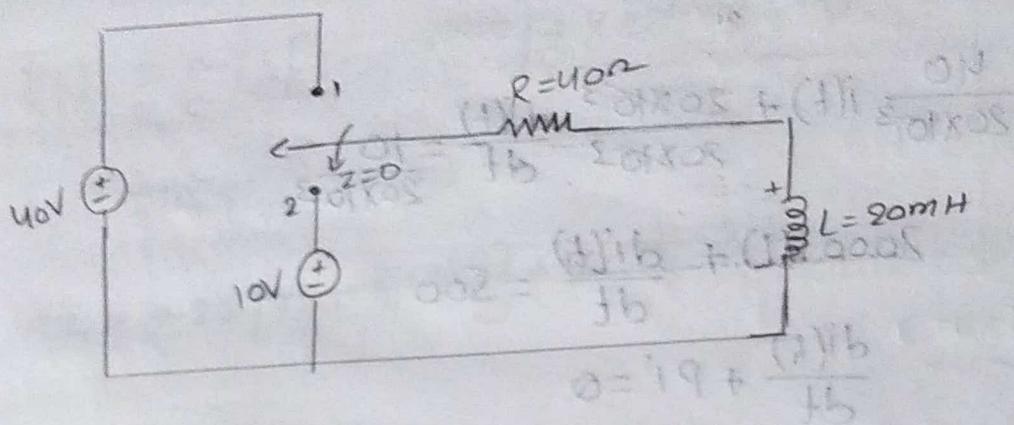The network shown in the fig is under study state condition with switch K is at position 1. find the expresss for $i(t)$ if switch is moved to position 2. Draw the variation of $i(t)$



At position 1

At $t=0^-$


$$i(0^-) = I_0 = \frac{V}{R} = \frac{10}{40} = 0.25 \text{ A}$$

$$= I_0 = \frac{40}{40} = 1 \text{ A}$$

At position 2

At $t \geq 0^+$

At switch is moved to position 2

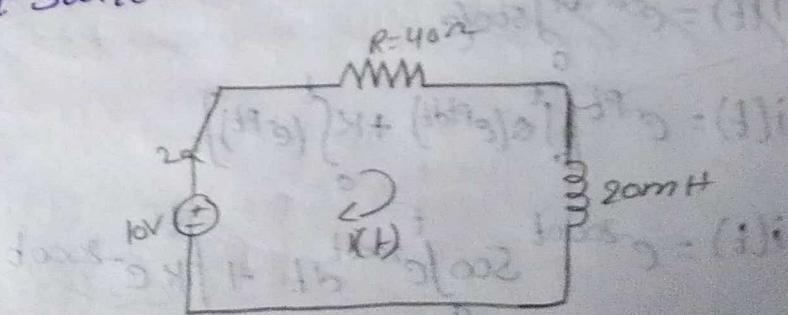

Applying KVL


$$10 - 40i(t) - 20 \frac{di(t)}{dt}$$

$$-40i(t) - 20 \frac{di(t)}{dt} = 10$$

$$-40i(t) - 20 \times 10^{-3} \frac{di(t)}{dt} + 10 = 0$$

Non-Homogeneous (RL Circuit)

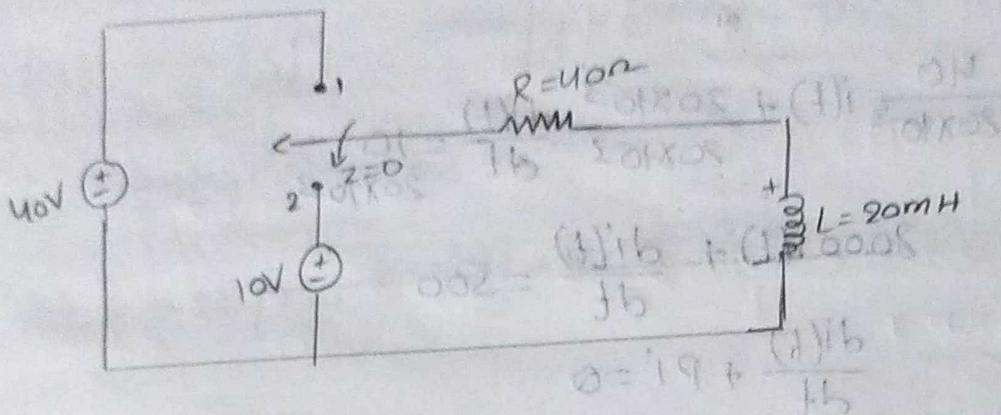The network shown in the fig is under study state condition with switch K is at position 1. find the expresssion for $i(t)$ if switch is moved to position 2. Draw the variation of $i(t)$



At Position 1

$$i(0^-) = I_0 = \frac{V}{R} = i(0^+)$$

$$= I_0 = \frac{40}{40} = 1A$$


$$002 = 1$$

$$002 = 0$$

At Position 2 (position - non resistive circuit so it's initial value is 0)

$$At t \geq 0^+ \quad i(t) = (1 + (t/t_{\text{ind}}))i_0 = (1 + (t/0.05))1 = (1 + 20t)$$

At switch is moved to Position 2

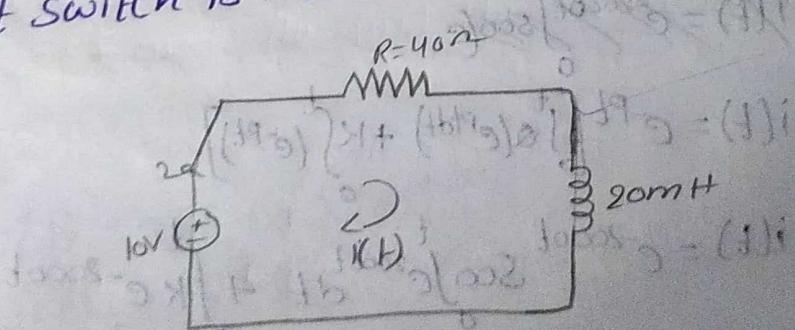

Applying KVL

$$10 - 40i(t) - 20 \frac{di(t)}{dt}$$

$$-40i(t) - 20 \frac{di(t)}{dt} = 10$$

$$-40i(t) - 20 \times 10^{-3} \frac{di(t)}{dt} + 10 = 0$$

$$40i(t) + 20 \times 10^{-3} \frac{di(t)}{dt} = 10$$

Standard form of first order non-homogeneous differential eqn
is given by

$$\frac{di(t)}{dt} + Pi = Q$$

$$\frac{40}{20 \times 10^{-3}} i(t) + \frac{20 \times 10^{-3}}{20 \times 10^{-3}} \frac{di(t)}{dt} = \frac{10}{20 \times 10^{-3}}$$

$$2000 i(t) + \frac{di(t)}{dt} = 500$$

$$\frac{di(t)}{dt} + P i = Q$$

Compare the above equation with standard form of
first order non-homogeneous D.E.

$$P = 2000$$

$$Q = 500$$

The solution for first order non-homogeneous D.E is given by

$$i(t) = e^{-Pt} \int_0^t Q(e^{Pdt}) K(e^{-Pt}) dt$$

$$i(t) = e^{-2000t} \int_0^t 500 e^{2000t} dt$$

$$i(t) = e^{-2000t} \left[\int_0^t Q(e^{Pdt}) dt + K \int_0^t (e^{-Pt}) dt \right]$$

$$i(t) = e^{-2000t} \int_0^t 500 e^{2000t} dt + \int_0^t K e^{-2000t} dt$$

$$= 500 e^{-2000t} \left[\frac{e^{2000t}}{2000} \right]_0^t + K e^{-2000t}$$

$$= 500 e^{-2000t} \left[\frac{e^{2000t}}{2000} - \frac{1}{2000} \right] + K e^{-2000t}$$

$$= 500 e^{-2000t} \frac{1}{2000} \left[e^{2000t} - 1 \right] + K e^{-2000t}$$

$$\begin{aligned}
 &= \frac{500}{2000} e^{-2000t} [e^{2000} - 1] + K e^{-2000t} \\
 &= 0.25 e^{-2000t} [e^{2000} - 1] + K e^{-2000t} \\
 &= 0.25 \left[\frac{e^{2000}}{e^{-2000}} - e^{-2000t} \right] + K e^{-2000t} \\
 i(t) &= 0.25 [1 - e^{-2000t}] + K e^{-2000t} \quad \text{--- (1)}
 \end{aligned}$$

At $t=0 \Rightarrow$ initial conditions

$$i(0) = 0.25 [1 - e^{-2000(0)}] + K e^{-2000(0)}$$

$$I_0 = 0 + K$$

$$I_0 = K$$

$$\boxed{K=1}$$

Sub in eq (1)

$$i(t) = 0.25 [1 - e^{-2000t}] + e^{-2000t}$$

$$i(t) = 0.25 e^{-2000t} (1 + e^{-2000t})$$

$$i(t) = 0.25 + 0.75 e^{-2000t}$$

$$t=T$$

$$t=1T$$

$$i(t) = 0.25 + 0.75 e^{-2000(1)}$$

$$i(t) = 0.25 + 0$$

$$i(t) = 0.25$$


$$0 = 0.25 + (1) \cancel{A} - (1) \cancel{0.25} = 0$$

$$0 = 0.25 + (1) \cancel{A} - (1) \cancel{0.25}$$

$$0 = 0.25 + (1) \cancel{A} - (1) \cancel{0.25} (1 - 0.25) = 0$$


Non-Homogenous (RC-circuit)

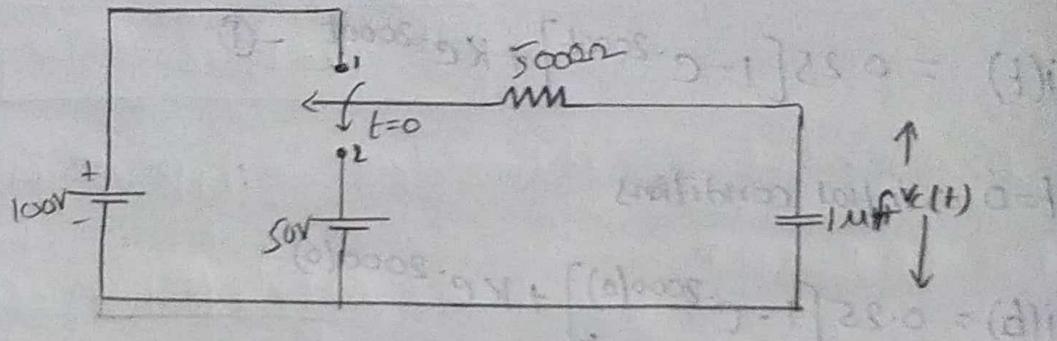The switch is moved from position 1 to position 2 and at
and find the voltages $v_c(t)$ and $v_r(t)$ for $t > 0$



At Position 1

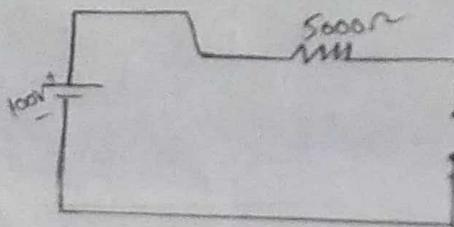
At $t=0^-$ position switch is connected to Position



$$v(0^-) = v_0 = v_0(0^+) = 100V$$

At Position 2

At $t \geq 0^+$

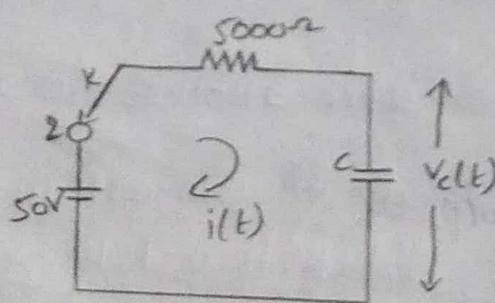

The current through the resistor and capacitor both are same

$$v_i(t) = i(t)$$

Applying KVL

$$50 - 5000i(t) - v_c(t) + 50 = 0$$

$$-5000c \frac{dv_c(t)}{dt} - v_c(t) + 50 = 0$$

$$-5000(1 \times 10^{-6}) \frac{dv_c(t)}{dt} - v_c(t) + 50 = 0$$

$$-(5 \times 10^{-3})(1 \times 10^6) \frac{dv_c(t)}{dt} - v_c(t) + 50 = 0$$

$$\cancel{-(5 \times 10^{-3})} \cancel{I} \quad 5 \times 10^{-3} \frac{dv_c(t)}{dt} + v_c(t) = 50$$

(Applying KVL) $\frac{dv_c(t)}{dt} + 200v_c(t) = 10,000$

$$-5000i(t) - \cancel{v_c(t)} + 50 = 0$$

$$-5000i(t) - C \cdot \cancel{\frac{dv_c(t)}{dt}} + 50 = 0$$

$$-5000i(t) - (1 \times 10^{-6}) \cdot \frac{dv_c(t)}{dt} = -50$$

(Note: (II)T - (III)

The standard form of the first order non-homogeneous

DE

$$\frac{dv}{dt} + Pv = Q$$

$$\frac{dV_c(t)}{dt} + 200V_c(t) = 10,000$$

Compare this in above equation

$$P = 200, Q = 10,000$$

$$V_c(t) = e^{-Pt} \int^t_0 Q e^{Pt} dt + K \cdot e^{-Pt}$$

$$V_c(t) = e^{-200t} \int^t_0 10,000 e^{200t} dt + K \cdot e^{-200t}$$

$$V_c(t) = e^{-200t} \cdot 10,000 \left[\frac{e^{200t}}{200} \right]_0^t + K \cdot e^{-200t}$$

$$V_c(t) = e^{-200t} \cdot 10,000 \left[\frac{e^{200t}}{200} - \frac{1}{200} \right] + K \cdot e^{-200t}$$

$$V_c(t) = e^{-200t} \cdot \frac{10,000}{200} \left[e^{200t} - 1 \right] + K \cdot e^{-200t}$$

$$V_c(t) = e^{-200t} \cdot 50 \left[1 - e^{-200t} \right] + K \cdot e^{-200t}$$

At $t=0$

$$V_c(t) = e^{-200(0)} \cdot 50 \left[1 - e^{-200(0)} \right] + K \cdot e^{-200(0)}$$

$$V_c(t) = K \Rightarrow K = 100$$

$$V_C(t) = 50(1 - e^{200t}) + 100e^{-200t}$$

$$V_C(t) = 50 - 50(e^{200t}) + 100e^{-200t}$$

$$V_C(t) = 50 + 50e^{-200t}$$

$$\boxed{V_C(t) = 50(1 + e^{-200t})}$$

$$V_R(t) = R \times i(t)$$

$$V_R(t) = (1 \times 10^6) \frac{dV_C(t)}{dt}$$

$$V_R(t) = R(-0.01e^{-200t})$$

$$= 5000(-0.01e^{-200t})$$

$$I(t) = I_C(t) = I_R(t)$$

$$I_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$= (1 \times 10^{-6}) \frac{d}{dt} [50(1 + e^{-200t})]$$

$$V_R(t) = -50e^{-200t}$$

$$= (1 \times 10^{-6}) \left(50 \frac{d}{dt} + 50 \frac{d}{dt} e^{-200t} \right)$$

$$= (1 \times 10^{-6}) [0 + 50(-200)e^{-200t}]$$


$$= (1 \times 10^{-6}) (1 \times 10^{-3}) e^{-200t}$$

$$= (1 \times 10^{-3}) e^{-200t}$$

$$= 0.01e^{-200t}$$

Response of source free series R-L-C circuit:

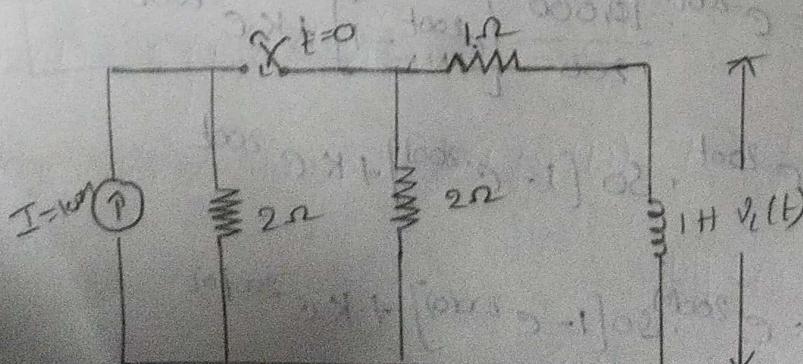Initially in the circuit the switch 'K' is kept open for very long time. At $t=0$ it is closed find the expression for $i(t)$ for $t > 0$ and also find voltage across the inductor $V_L(t)$. Sketch $i(t)$ and $V_L(t)$




At position A $t=0^-$



$$i(0^-) = I_0 = I(0^+) = 0$$

At Position B


$t > 0$

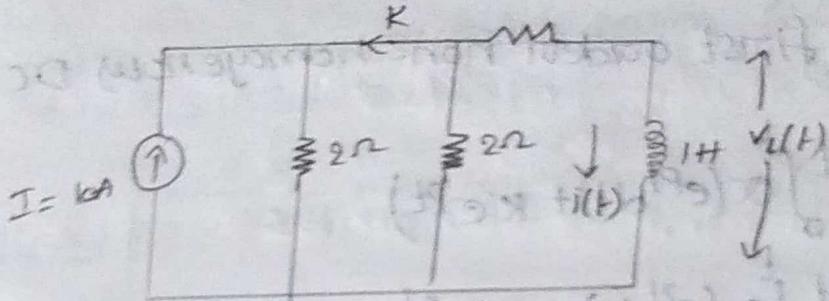
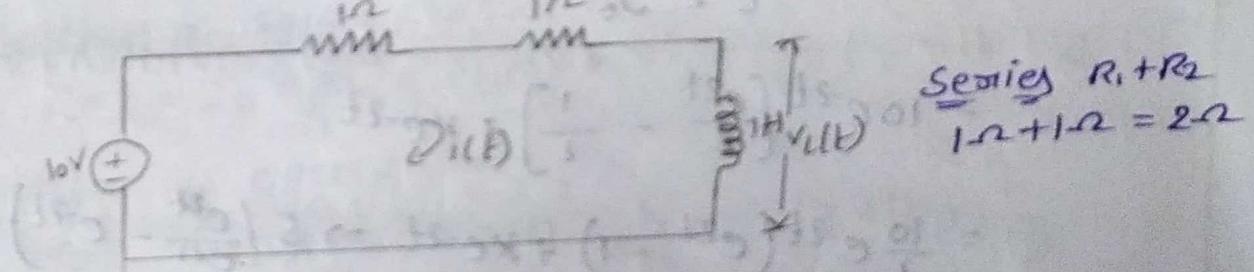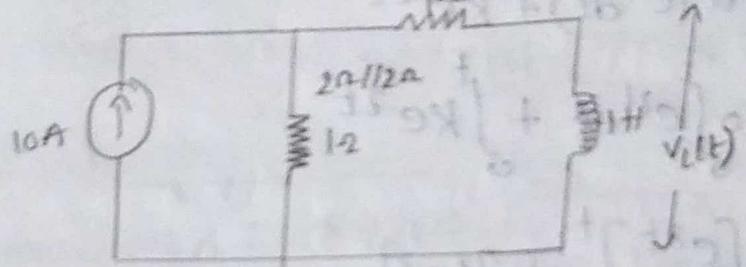
$$\frac{2 \cdot 2}{2+2} = \frac{4}{4} = 1\Omega$$


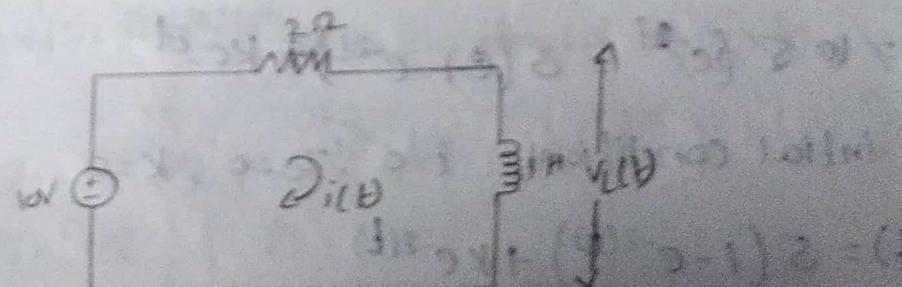
$$\text{Series } R_1 + R_2 \\ 1\Omega + 1\Omega = 2\Omega$$



By Applying KVL

$$-2i(t) - \frac{di(t)}{dt} + 10 = 0$$

$$+ \left(\frac{di(t)}{dt} + 2i(t) \right) = -10$$

$$\frac{di(t)}{dt} + 2i(t) = 10$$

The standard form

$$\frac{di(t)}{dt} + pi(t) = q$$

compose this in above equation

$$P=2 \quad Q=10$$

The solution for first order non-homogeneous DE is given by

$$i(t) = e^{-Pt} \int_0^t Q(e^{Pt} dt) + K e^{-Pt}$$

$$i(t) = e^{-2t} \int_0^t 10(e^{2t} dt) + K e^{-2t}$$

$$= e^{-2t} \left[10 \int_0^t e^{2t} dt \right] + \int_0^t K e^{-2t}$$

$$= 10e^{-2t} \left[\frac{e^{2t}}{2} \right] + K e^{-2t}$$

$$= 10e^{-2t} \left[\frac{e^{2t}}{2} - \frac{1}{2} \right] + K e^{-2t}$$

$$= \frac{10}{2} e^{-2t} (e^{2t} - 1) + K e^{-2t} \Rightarrow 5 (e^{2t} - e^{-2t}) + K e^{-2t}$$

$$i(t) = 5(1 - e^{-2t}) + K e^{-2t}$$

At $t=0$ initial condition $i=0, I_0=0, K=0$

$$i(t) = 5(1 - e^{-2t}) + K e^{-2t}$$


$$i(t) = 5(1 - e^{-2t}) + 0 \cdot (e^{-2t})$$

$$i(t) = 5(1 - e^{-2t})$$


Voltage across the inductor ($V_L(t)$) = $L \frac{di(t)}{dt}$

$$V_L(t) = L \frac{d}{dt} [5(1 - e^{-2t})] = [5(0 - e^{-2t})]$$

$$V_L(t) = 10e^{-2t} V$$

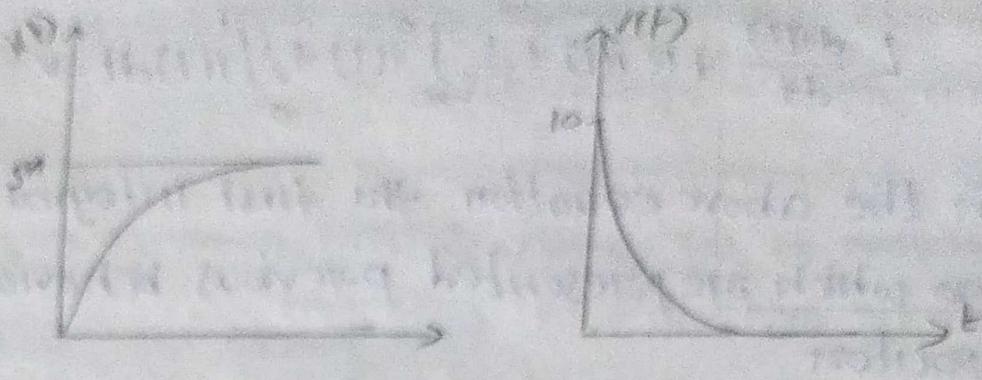

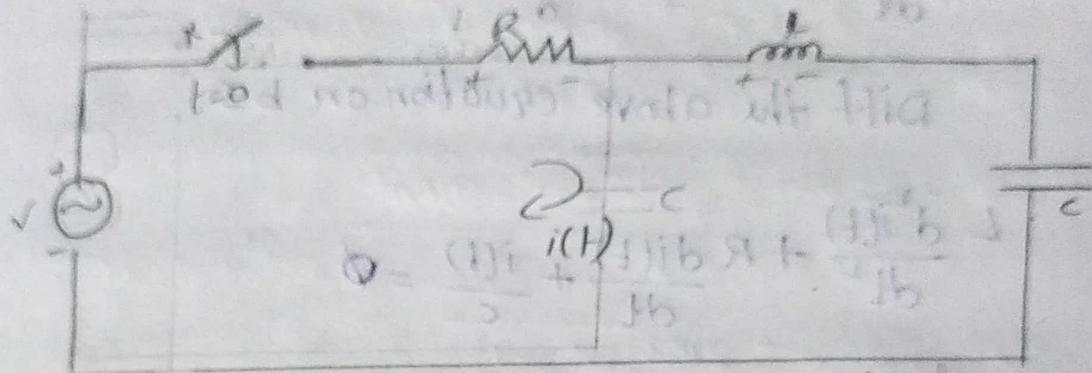Response of source free series RLC circuit:



$$\text{At position } A: \text{at } t(0^-); \frac{dV}{dt} + \frac{1}{L}i + \frac{1}{R}i + \frac{1}{C}i = 0$$


Inductor is short circuit

$$i(0^-) = I_0 \neq \frac{dV}{dt} = i(0^+) = 0$$

capacitor is open circuit

$$V(0^-) = V_0 \neq IR = V(0^+) = 0$$

$t \geq 0$ switch is closed

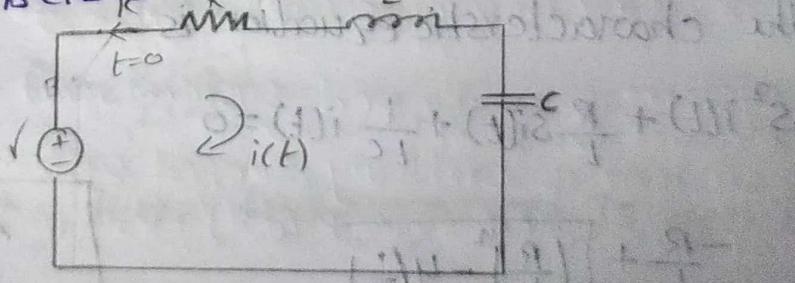

By applying KVL

$$-R(i(t)) - L \frac{di(t)}{dt} - \frac{1}{C} \int i(t) dt + V = 0$$

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt = V$$

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt = V$$

$$L \frac{di(t)}{dt} + R i(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt + \int_0^t i(t) dt = V$$

In the above equation the first integral part becomes zero which represented previous behaviour of the capacitor.

Now,

$$L \frac{di(t)}{dt} + R i(t) + \frac{1}{C} \int_0^t i(t) dt = V$$

Diff the above equation on b.s

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{i(t)}{C} = 0$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

To get the characteristic equation (or) auxiliary equation
Replace

$$\frac{d^2}{dt^2} \text{ with } s^2 \text{ and } \frac{d}{dt} \text{ with } s$$

Now the characteristic equation is

$$s^2 i(t) + \frac{R}{L} s i(t) + \frac{1}{LC} i(t) = 0$$

$$\frac{-\frac{R}{L} + \sqrt{\left(\frac{R}{L}\right)^2 - 4\left(\frac{1}{LC}\right)}}{2}$$

$$\therefore Ax^2 + Bx + C \\ -B \pm \sqrt{B^2 - 4ac} \\ \frac{2A}{2A}$$

$$s_{1,2} = \frac{-\frac{R}{L} + \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$s_{1,2} = \frac{-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

Responses are dependent on
roots nature
 $T_{trans} = \frac{1.10}{LC}$ in initial value 0

Before going to analysis the response of RLC circuit based on the roots of characteristic equations, we should define the following terms

* Critical Resistance: which is the value of resistance used to reduce the square root value to zero. This is denoted by R_{CR}

$$R_{CR} = \frac{1}{\sqrt{LC}}$$

$$R_{CR} = \frac{2L}{\sqrt{LC}}$$

$$R_{CR} = \frac{2\sqrt{L} \times \sqrt{C}}{\sqrt{L} \times \sqrt{C}}$$

$$R_{CR} = 2\sqrt{LC}$$

* Damping ratio: It is denoted by ξ^2

It is defined as actual resistance to the critical resistance

$$\xi^2 = \frac{R}{R_{CR}}$$

$$\xi^2 = \frac{R}{2(\sqrt{LC})}$$

$$\xi^2 = \frac{R}{2}(\sqrt{\frac{C}{L}})$$

* Un damped natural frequency: It is denoted by ω_n

It is defined as the oppose due to the circuit becomes 0, then the circuit is operating with natural frequency it is also called un damped natural frequency otherwise the system is operating with damping frequency denoted with ω_d

$$\omega_n = \text{natural frequency} = \frac{1}{\sqrt{LC}}$$

$$\text{damping frequency} (\omega_d) = \omega_n \sqrt{1 - 2\xi^2}$$

The standard form of 2nd order transfer function is given by $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$. The denominator polynomial of closed looped transfer function of 2nd order system when equating to zero is nothing but characteristic egn.

Characteristic egn is $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$

Let s_1, s_2 are the roots of characteristic egn then

$$\frac{-2\zeta\omega_n \pm \sqrt{(-2\zeta\omega_n)^2 - 4(1)\omega_n^2}}{2(1)}$$

$$\Rightarrow -2\zeta\omega_n \pm \frac{\sqrt{4\zeta^2\omega_n^2 - 4\omega_n^2}}{2}$$

$$\Rightarrow -2\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

$$\Rightarrow \frac{\cancel{2}(-2\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1})}{\cancel{2}}$$

$$\Rightarrow -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

$$s_1 = -\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1}; s_2 = -\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1}$$

where damping frequency (ω_d) = $\omega_n\sqrt{1 - \zeta^2}$

If $\zeta = 0$ system is undamped system roots are purely imaginary response is $K_1 e^{j\omega_n t} + K_2 e^{-j\omega_n t}$
when $\zeta = 1$ system is critically damped system roots are real and equal \Rightarrow response = $K_1 e^{-t} + K_2 t e^{-t}$

when $\zeta > 1$ system is overdamped system roots are real and unequal response is $K_1 e^{-s_1 t} + K_2 e^{-s_2 t}$

when $0 < \zeta < 1$ system is underdamped system roots are complex and conjugate. response = $K_1 e^{-\zeta\omega_n t} \cos(\omega_d t) + K_2 e^{-\zeta\omega_n t} \sin(\omega_d t)$

The general egn of characteristic egn is given by

$$i(t) = K_1 e^{(-\alpha + j\omega_d)t} + K_2 e^{(-\alpha - j\omega_d)t}$$


The response of RLC circuit can be written in another form

$$i(t) = K_1 e^{st} + K_2 t e^{st}$$

where $\omega = \sqrt{\omega_n}$; $\omega_n = \sqrt{1 - \frac{R^2}{L^2}}$

Note: $e^{j\theta} = \cos\theta + j\sin\theta$

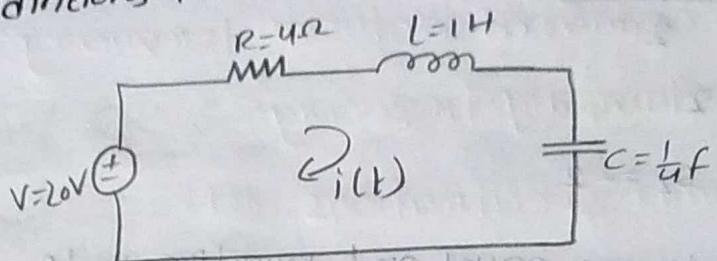find the expression for current in RLC series circuit fed by DC voltage of 20V with $R=4\Omega$, $L=1H$, $C=\frac{1}{4}F$. Assume initial conditions to be zero.



At position A ($t=0^-$):

$$I(0^-) = I_0 = I(0^+) = 0$$

$$v(0^-) = v_0 = v(0^+) = 0$$

Applying KVL to the above circuit

$$-4i(t) - 1 \frac{di(t)}{dt} - 4 \int i(t) dt + 20 = 0$$

$$\frac{di(t)}{dt} + 4i(t) + 4 \int i(t) dt = 20$$

$$\frac{di(t)}{dt} + 4i(t) + \int_{-\infty}^t 4 \int i(t) dt dt = 20$$

$$\frac{di(t)}{dt} + 4i(t) + \int_{-\infty}^0 i(t) dt + \int_0^t 4 \int i(t) dt dt = 20$$

This is in the form of integro differential eqn

$$\frac{di(t)}{dt} + 4i(t) + \int_0^t 4 \int i(t) dt dt = 20 \quad \text{--- (1)}$$

Differentiate the above eqn

$$\frac{d^2i(t)}{dt^2} + 4 \frac{di(t)}{dt} + 4i(t) = 0 \quad \text{--- (2)}$$

To get the characteristic eqn (2) auxiliary eqn replace $\frac{d^2}{dt^2}$ with s^2 and $\frac{di}{dt}$ with s

Now, the characteristic eqn is

$$s^2 + 4s + 4 = 0$$

This is in the form of $Ax^2 + Bx + C = 0$

$$s^2 i(t) + 4s i(t) + 4i(t) = 0$$

$$s^2 i(t) + 4s i(t) + 4i(t) = 0$$

$$s_{1,2} = \frac{-4 \pm \sqrt{16 - 4(1)(4)}}{2(1)}$$

$$= \frac{-4 \pm \sqrt{0}}{2}$$

$$= -2$$

$$s_1 = -2 \quad s_2 = -2$$

PFQ = This roots are equal and negative roots

$$i(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$i(t) = K_1 e^{-2t} + K_2 - t e^{-2t}$$

~~$$= K_1 e^{-2t} + K_2 e^{-2t}$$~~

Taking initial condition $t=0$

initial condition $t=0$

~~$$i(0) = K_1 e^{-2(0)} + K_2 e^{-2(0)}$$~~

$$i(0) = K_1 e^{-2(0)} + K_2 \cdot 0 e^{-2(0)}$$

~~$$i(0) = K_1 e^0 + K_2 e^0$$~~

$$i(0) = K_1 e^0 + 0$$

~~$$i(0) = K_1 + K_2$$~~

$$i(t) = K_1 e^{-2t} + K_2 - t e^{-2t}$$

~~$$K_1 = -K_2$$~~

~~$$K_2 = -K_1$$~~

$$i(t) = 0 + K_2 t e^{-2t}$$

$$i(t) = K_2 t e^{-2t}$$

sub initial values in eqn ①

$$\frac{di(0)}{dt} + 4i(0) + 4 \int i(0) dt = 20$$

$$\frac{di(0)}{dt} = 0 + 0 + 0 = 0$$

$$\frac{di(t)}{dt} = K_2 [t(-2)e^{-2t} + e^{-2t}(1)]$$

Taking initial conditions $i(t)=0$ & $t=0$

$$\frac{di(0)}{dt} = K_2 [0(-2)e^{-2(0)} + e^{-2(0)}]$$

$$20 = K_2$$


$$i(t) = K_1 e^{-5t} + K_2 e^{-2t}$$

$$= 0 + 20 e^{-2t}$$

$$i(t) = 20 e^{-2t}$$

Three Domains

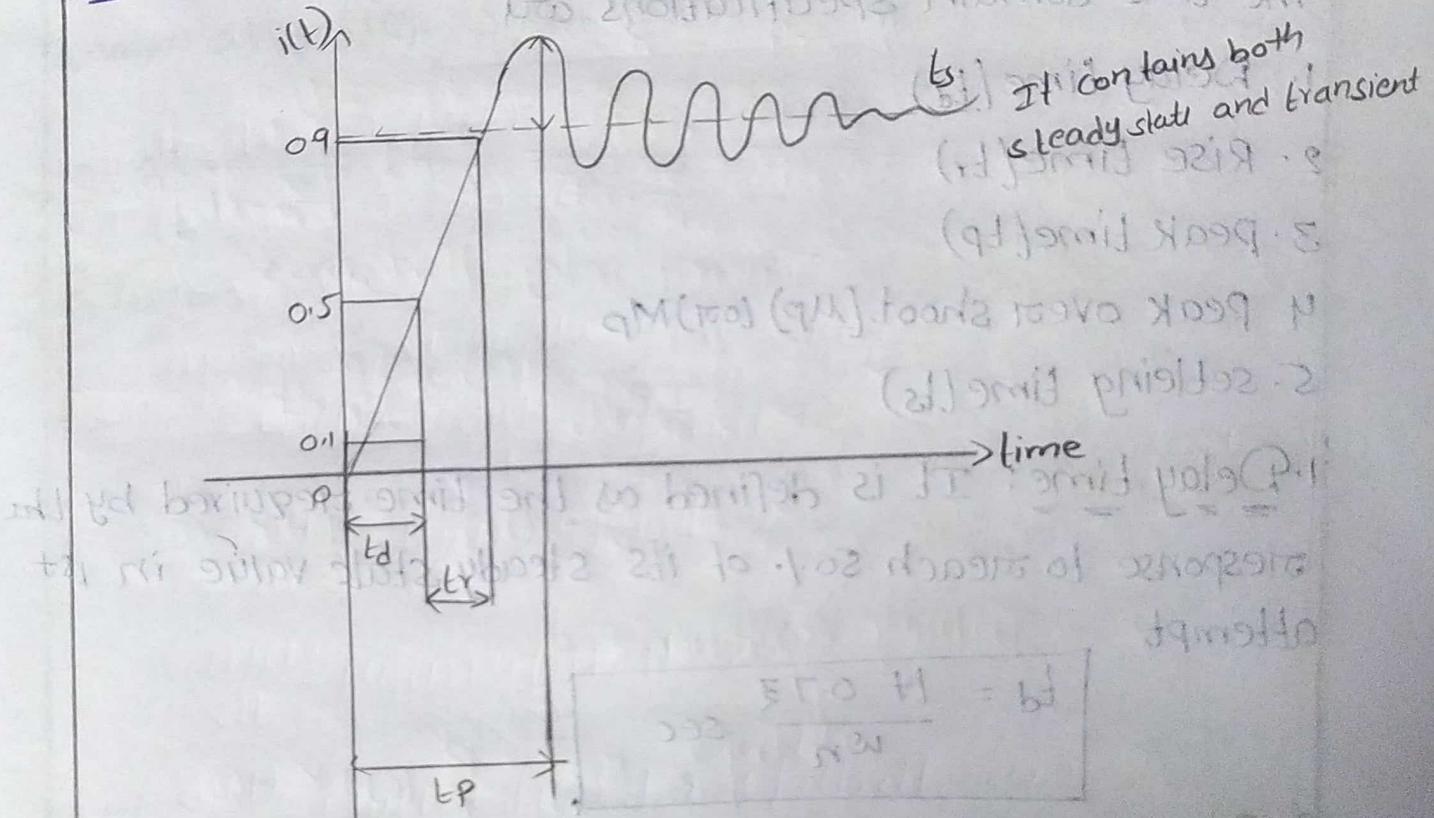The Response of RLC second order circuit:



Specifications:

→ Delay time (t_d)

→ Rise time (t_r)

→ Peak time (t_p)

→ Peak overshoot (u_p)


→ Settling time (t_s)

$$\frac{3 - \pi^2}{b^2} = 1$$

The response of second order RLC circuit for unit step input is given by

$$i(t) = I_{ss} - \frac{e^{-\zeta \omega_n t}}{\sqrt{1 - \zeta^2}} [\sin \omega_d t + \theta]$$

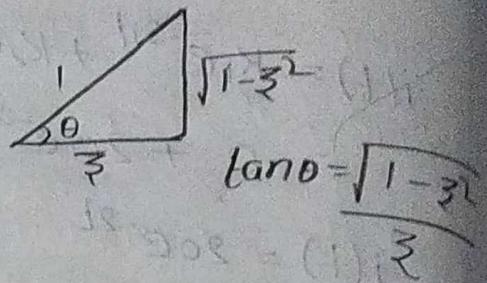where $\theta = \tan^{-1} \left[\frac{\sqrt{1 - \xi^2}}{\xi} \right]$



where ξ is the damping ratio.

ω_n is undamped natural frequency

ω_d is damping frequency

The time domain specifications are

1. Delay time (t_d)
2. Rise time (t_r)
3. Peak time (t_p)
4. Peak overshoot (M_p) ($10\% M_p$)
5. Settling time (t_s)

1. Delay time: It is defined as the time required by the response to reach 50% of its steady state value in 1st attempt

$$t_d = \frac{1 + 0.7\xi}{\omega_n} \text{ sec}$$

2. Rise time: It is defined as the time required by the response to rise from 10% to 90% of its final value

$$t_r = \frac{\pi - \theta}{\omega_d}$$

$$t_r = \frac{\pi - \tan^{-1} \sqrt{1 - \xi^2}/\xi}{\omega_d}$$

3. Peak time: It is defined as the time at which peak overshoot occurs is known as peak time

$$t_p = \frac{\pi}{\omega_d}$$

4. Peak over shoot: The amount by which the response over shoots its final value is known as Peak over shoot expressed in percentage form.


$$M_p(0\%) M_p = e^{-3\pi/\sqrt{1-3^2}}$$

$$\therefore M_p = e^{-3\pi/\sqrt{1-3^2}} \times 100$$

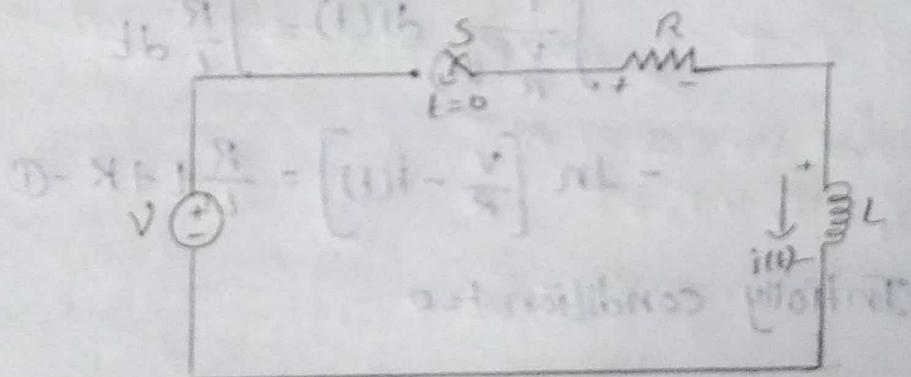5. Settling time: The time required for the response to decrease and becomes steady at its steady state value is known as settling time

$$t_s = \frac{4}{3} \omega_n \text{ sec}$$

Response of RL series circuit with Source:



$$\text{At } t=0^- \quad v = X + (0) - \frac{V}{R} = [0] - \frac{V}{R}$$

$$i(0^-) = i(0^+) = \frac{V}{R}$$

$$I(0^-) = I_0 = I_0(0^+) = \frac{V}{R}$$

$I_0 \rightarrow$ Max value of initial current

At $t \geq 0^+$ switch is closed

By applying KVL:

$$-i(t)R - L \cdot \frac{di(t)}{dt} + V = 0$$

In this condition voltage source is introduced now

Applying KVL

$$-i(t)R - L \cdot \frac{di(t)}{dt} + V = 0$$

4. Peak overshoot: The amount by which the response overshoots its final value is known as peak overshoot expressed in percentage form


$$\text{O.P. (per cent)} = e^{-\frac{R}{2L}} \times 100$$

$$1. \text{ O.P.} = e^{-\frac{R}{2L}} \times 100$$

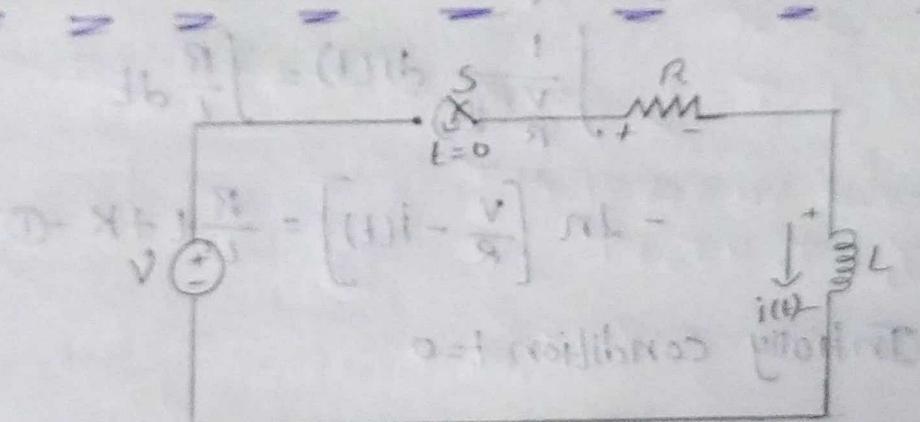5. Settling Time: The time required for the response to decrease and becomes steady at its steady state value is known as settling time

$$T_s = \frac{4}{3} \frac{L}{R} \text{ sec.}$$

Response of RL series circuit with Source:



$$\text{At } t=0^+ = X + (0) \frac{R}{L} - \left[(0)I_0 + \frac{V}{R} \right] \text{ sec.}$$

$$i(0^+) = i(0^-) \Rightarrow \frac{V}{R}$$

$$I(0^+) = I_0 = I_0(0^+) = \frac{V}{R}$$

$I_0 \rightarrow$ Max value of initial current

At $t \geq 0^+$ switch is closed

By applying KVL:

$$-i(t)R - L \cdot \frac{di(t)}{dt} + V = 0$$

In this condition voltage source is introduced now

(Applying KVL)

$$-i(t)R - L \cdot \frac{di(t)}{dt} + V = 0$$

$$v + i(t)R + L \frac{di(t)}{dt} = V$$

divide R in b.s

$$\frac{R}{L} i(t) + \frac{di(t)}{dt} = \frac{V}{L}$$

$$\frac{R}{R} i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V}{R}$$

$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V}{R}$$

$$\frac{L}{R} \frac{di(t)}{dt} = \frac{V}{R} - i(t)$$

$$\frac{di(t)}{dt} = \frac{R}{L} i(t) - \frac{V}{R}$$

Taking integration on b.s

$$\int \frac{1}{\frac{V}{R} - i(t)} di(t) = \int \frac{R}{L} dt$$

$$-\ln \left[\frac{V}{R} - i(t) \right] = \frac{R}{L} t + K \quad \textcircled{1}$$

Initially condition $t=0$

$$-\ln \left[\frac{V}{R} - i(0) \right] = \frac{R}{L} (0) + K \quad \textcircled{2}$$

$$\text{sub } K \text{ in eq } \textcircled{1} \quad K = -\ln \left(\frac{V}{R} \right)$$

$$-\ln \left[\frac{V}{R} - i(t) \right] = \frac{R}{L} t - \ln \left(\frac{V}{R} \right)$$

$$-\left[\ln \left(\frac{V}{R} - i(t) \right) - \ln \left(\frac{V}{R} \right) \right] = \frac{R}{L} t$$


$$-\ln \left[\frac{\frac{V}{R} - i(t)}{\frac{V}{R}} \right] = \frac{R}{L} t$$

$$\frac{\frac{V}{R} - i(t)}{\frac{V}{R}} = e^{\frac{R}{L} t}$$

$i(t) = \left(\frac{V}{R}\right) - \left(\frac{V}{R}\right) e^{-Rt}$
 In the above equation we can observe that, it is a first order non-homogeneous D.E and it is a combination of both steady state response and Transient response. Steady state response is also known as force response it is denoted by $\frac{V}{R}$ similarly transient response is denoted by $\left(\frac{V}{R}\right) e^{-Rt}$

$\frac{V}{R} e^{Rt}$ which is also known as 'a input response'. Time constant $T = \frac{L}{R}$ for RL series circuit. For different values of t ($t = T, 2T, 4T, 6T, \dots$) the response $i(t) = 0.99$

$$i(t) = 0.99$$

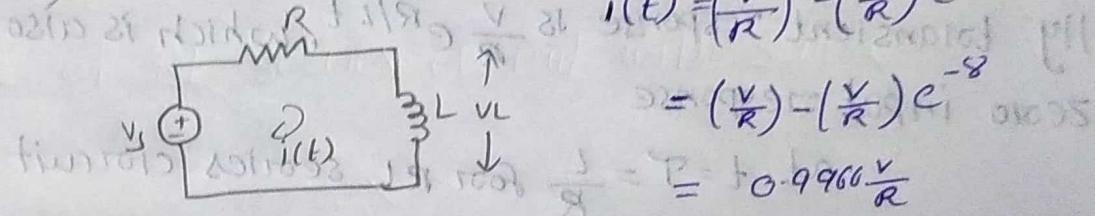

$$i(t) = \left(\frac{V}{R}\right) - \left(\frac{V}{R}\right) e^{-Rt}$$

$$= \left(\frac{V}{R}\right) - \left(\frac{V}{R}\right) e^{-\frac{t}{T}}$$

$$= P + 0.99e^{-\frac{t}{T}}$$

By applying KVL

$$v_s = R i(t) - L \frac{di(t)}{dt} = 0$$

$$v_s - L \frac{di(t)}{dt} = R i(t)$$

Divide the both sides with 'R'

$$\frac{V}{R} - \frac{L}{R} \frac{di(t)}{dt} = i(t)$$

$$-\frac{L}{R} \frac{di(t)}{dt} = \frac{-V}{R} + i(t)$$


$$\frac{di(t)}{i(t) - \frac{V}{R}} = -\frac{R}{L} dt$$

Integrating on L.S

$$\int \frac{di(t)}{i(t) - \frac{V}{R}} = \int -\frac{R}{L} dt$$

$$\ln(i(t) - \frac{V}{R}) = -\frac{R}{L} t + R$$
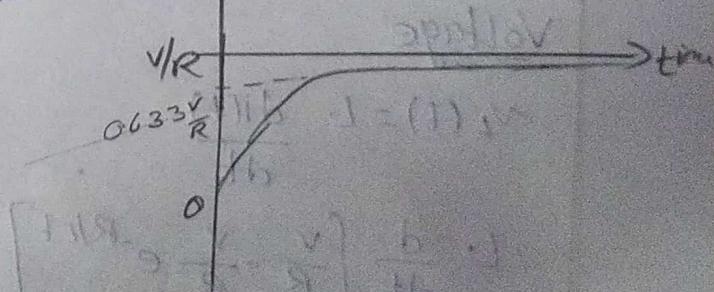
$$\ln \frac{i(t) - \frac{V}{R}}{\frac{V}{R}} = -\frac{R}{L} t$$



$$III) \frac{V}{R} = C \cdot R \cdot i(t)$$

$$III) \frac{V}{R} = \frac{R}{L} e^{-R/L t}$$

$$III) \frac{V}{R} e^{-R/L t} + \frac{V}{R}$$

$$i(t) = \frac{V}{R} + C \cdot e^{-R/L t} \cdot \frac{R}{L}$$

In the above eqn we can observe that it is a first order Non-Homogeneous D.E and it is a combination of both steady state response and transition response.

Steady state response is also a forced response as v₀ is zero input response.

at $t = T = \frac{L}{R}$ for RL series circuit

for different values of $N T$

$$t = T, 2T, 4T, 6T$$

$$\text{the response } i(t) = 0.9975 \frac{V}{R}$$

Voltage

$$v_L(t) = L \cdot \frac{di(t)}{dt}$$


$$L \cdot \frac{d}{dt} \left[\frac{V}{R} - \frac{V}{R} e^{-R/L t} \right]$$

L

$$v_L(t) = V \cdot e^{-R/L t} \text{ Volts}$$

$$(II) i = \frac{(I) i_b}{t_b} \cdot \frac{t}{t_b} - \frac{V}{R}$$
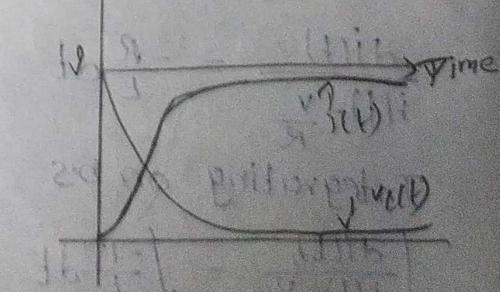
$$(II) i = \frac{V}{R} - \frac{(I) i_b}{t_b} \cdot \frac{t}{t_b}$$



If you consider i_0 (initial values of max current through the inductor before switching the expression of $i(t)$) can be written as $\frac{V}{R} - \left(\frac{V}{R} - i_0 \right) e^{-R/L t}$

$$i(t) = \frac{V}{R} e^{-R/Lt}$$

$$i(t) = \frac{V}{R} + \frac{R}{L} e^{-R/Lt}$$

$$i(t) = \frac{V}{R} e^{-R/Lt} + \frac{V}{R}$$

$$i(t) = \frac{V}{R} + C e^{-R/Lt}$$

In the above eqn we can observe that it is a first order Non-Homogeneous D.E and it is a combination of both steady state response and transition response.

Steady state response is also a forced response is $\frac{V}{R}$
The transient response is $\frac{V}{R} e^{-R/Lt}$, which is also known as zero input response

at $t = T = \frac{L}{R}$ for RL series circuit

for different values of nT

$$t = T, 2T, 4T, 6T$$

$$\text{the response } i(t) = 0.9975 \frac{V}{R}$$


Voltage

$$v_L(t) = L \frac{di(t)}{dt}$$

$$L \cdot \frac{d}{dt} \left[\frac{V}{R} - \frac{V}{R} e^{-R/Lt} \right]$$

L
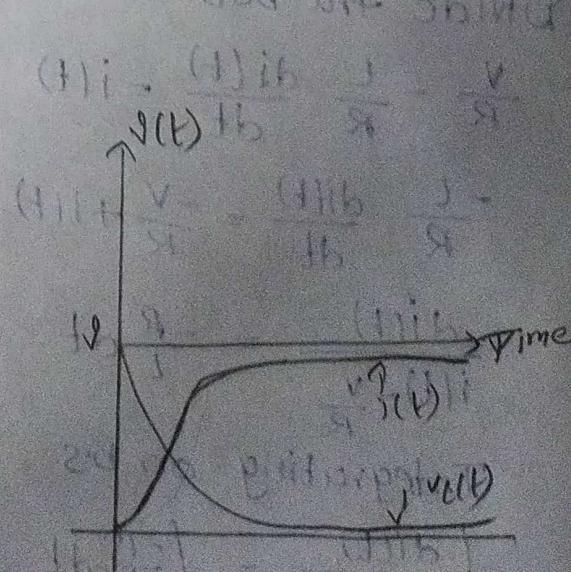
$$v_L(t) = V \cdot e^{-R/Lt} \text{ Volts}$$




If you consider i_0 (initial values of max current through

$$V_L(t) = (V - I_0 R) e^{-Rt/C}$$

voltage across the current

Response of RC circuit with source:

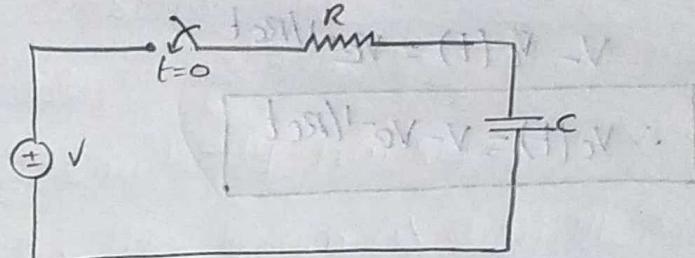

At $t=0^-$:

switch is in open condition
 $V(0^-) = V_0 = V(0^+)$

At $t \geq 0$:

switch is at closed condition

By applying KVL

$$-i(t)R - V_C(t) + V = 0$$

$$\text{where } i_C(t) = C \frac{dV_C(t)}{dt}$$

$$-C \frac{dV_C(t)}{dt} R - V_C(t) + V = 0$$

$$\Rightarrow C \frac{dV_C(t)}{dt} R = V - V_C(t)$$

$$\frac{dV_C(t)}{V - V_C(t)} = \frac{1}{RC} dt$$

Integrating on B.S

$$\int \frac{dV_C(t)}{V - V_C(t)} = \int \frac{1}{RC} dt$$


$$-\ln[V - V_C(t)] = \frac{1}{RC} t + K - ①$$

Applying Initial condition $t=0$;

$$-\ln[V - V_C(0)] = \frac{1}{RC} (0) + K$$

$$① \Rightarrow -\ln[V - V_C(t)] = \frac{1}{RC} t - \ln[V]$$
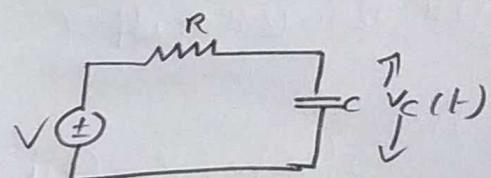
$$-\ln[V - V_C(t)] + \ln[V] = \frac{1}{RC} t$$



$$-\left[\ln\left(\frac{V-V_C(t)}{V}\right)\right] = \frac{1}{RC}t$$

$$\frac{V-V_C(t)}{V} = e^{-1/RCt}$$

$$V - V_C(t) = Ve^{-1/RCt}$$

$$\therefore V_C(t) = V - Ve^{-1/RCt}$$