

## UNIT - 2

### FREQUENCY RESPONSE

Resonance : Resonance is the phenomenon at which both

Voltage and Current are inphase.

→ At resonance total Circuit acts as resistive Circuit.

→ Power factor of the Circuit = 1 i.e., Unity power factor(UPF).

Resonant frequency : The frequency with which resonance occurs  
are Known as Resonant frequency. (or)

The frequency at which Capacitive reactance ( $x_c$ ) is equal to  
inductive reactance ( $x_L$ ) i.e.,  $x_c = x_L$  is called resonant  
frequency. Units : Hz

Applications : It is used in Radio station at receiving  
Sides. Basically we are having two types.

(i) Series Resonance.

(ii) Parallel Resonance.

(i) Series Resonance : Consider a Circuit having Resistance,  
Inductance, Capacitance Connected in Series, Excited with  
an alternating Voltage 'V'.

Here total impedance of Circuit  $Z = R + j(x_L - x_c)$

By Varying Supply frequency at some frequency the reactance of the circuit is equal to zero.


Capacitive Reactance ( $x_c$ ) is equal to Inductive reactance ( $x_L$ ) this is called Resonant Condition.

$$\therefore Z = R$$

$\therefore$  Total Circuit act as Resistive Ckt

$$\therefore x_L - x_C = 0$$

$$x_L = x_C$$

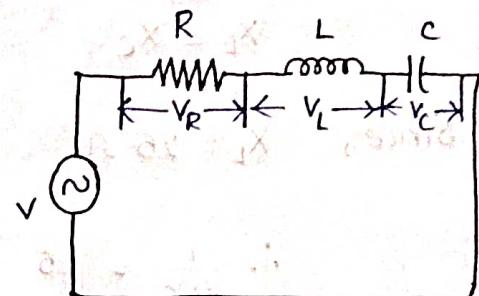

$$\omega_L = \frac{1}{\omega_C}$$

$$\omega^2 LC = 1$$

$$\omega^2 = \frac{1}{LC} \Rightarrow (2\pi f)^2 = \frac{1}{LC}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

'fr' is known as Resonant frequency.

Phasor Diagram:

$V_L$

$V_R$  At Resonance

$I$

$V_R$

$I$

$$V_L = V_C$$

$$\therefore x_L = x_C$$

$x_L$

$R$

$x_C$

$$\therefore x_L = x_C$$

$$Z = R$$

$Z = R$  at Resonance.

$x_L = x_C$ , So the Voltage drop across the L and C is

Zero and Current is Maximum and 'z' is minimum.

Problems:

1. For the Circuit shown in Fig 4.18 determine the Value of Capacitive reactance and impedance at resonance.


Sol:- At resonance

$$x_L = x_C$$

Since,  $x_L = 25 \Omega$

$$\therefore \frac{1}{\omega C} = 25$$

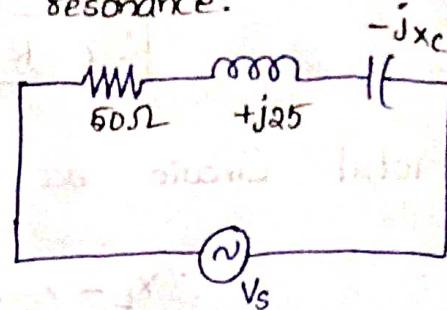The Value of impedance at resonance is  $Z = R$



2. Determine the resonant frequency for the circuit shown in Figure.


Sol:- The resonant frequency is

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{10 \times 10^{-6} \times 0.5 \times 10^{-3}}}$$

$$f_r = 2.25 \text{ KHz}$$


$$\therefore Z = 50 \Omega$$

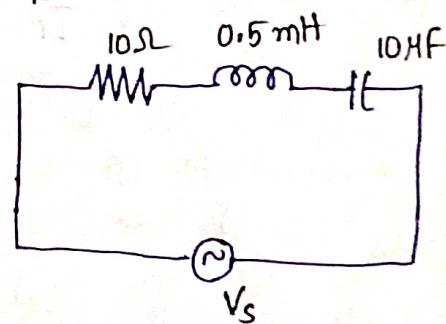

3. A  $50\Omega$  resistor is Connected in Series with an inductor having Internal resistance, a Capacitor and 100V Variable frequency Supply as shown in Fig. At a frequency of

200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants.

Sol:- At resonance, Current in the

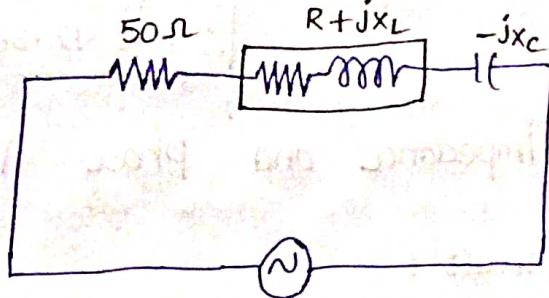

Circuit is maximum.

$$I = 0.7 \text{ A}$$

Voltage across Capacitor is  $V_C = I X_C$

$$\text{Since, } V_C = 200 \quad I = 0.7$$

$$X_C = \frac{1}{\omega C}$$

$$\omega C = \frac{0.7}{200}$$

$$C = \frac{0.7}{200 \times 2\pi \times 200}$$

$$C = 2.785 \text{ MF}$$

$$\text{At resonance } X_L - X_C = 0 \Rightarrow X_L = X_C$$

$$\text{Since, } X_C = \frac{1}{\omega C} = \frac{200}{0.7} = 285.7 \Omega$$

$$X_L = \omega L = 285.7 \Omega$$

$$\therefore L = \frac{285.7}{2\pi \times 200} = 0.23 \text{ H}$$

At resonance, the total impedance

$$Z = R + 50$$

$$\therefore R + 50 = \frac{V}{I} = \frac{100}{0.7}$$

$$R + 50 = 142.86 \Omega$$

$$\therefore R = 92.86 \Omega$$

Impedance and phase angle of a Series resonant

Circuit :

The Impedance of a Series RLC Circuit is

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

The variation of  $x_c$  and  $x_L$  with frequency is shown in figure.

At Zero frequency, both  $x_c$  and  $Z$  are infinitely large, and  $x_L$  is zero because at zero frequency the Capacitor act as an Open Circuit and the inductor act as a short circuit.

As the frequency increases,  $x_c$  decreases and  $x_L$  increases.

Since  $x_c$  is larger than  $x_L$ , at frequencies below the resonant frequency  $f_r$ ,  $Z$  decreases along with  $x_c$ . At resonant frequency  $x_c = x_L$ , and  $Z = R$ . At frequencies above the resonant frequency  $f_r$ ,  $x_L$  is larger than  $x_c$ , causing  $Z$  to increase. The phase angle as a function of frequency is shown in fig 4.2

At a frequency below the resonant frequency, Current leads the Source voltage because the Capacitive reactance is greater than the inductive reactance. The phase angle decreases as the frequency approaches the resonant value,

and is  $0^\circ$  at resonance. At frequencies above resonance, the current lags behind the source voltage, because the inductive reactance is greater than capacitive reactance. As the frequency goes higher, the phase angle approaches  $90^\circ$ .

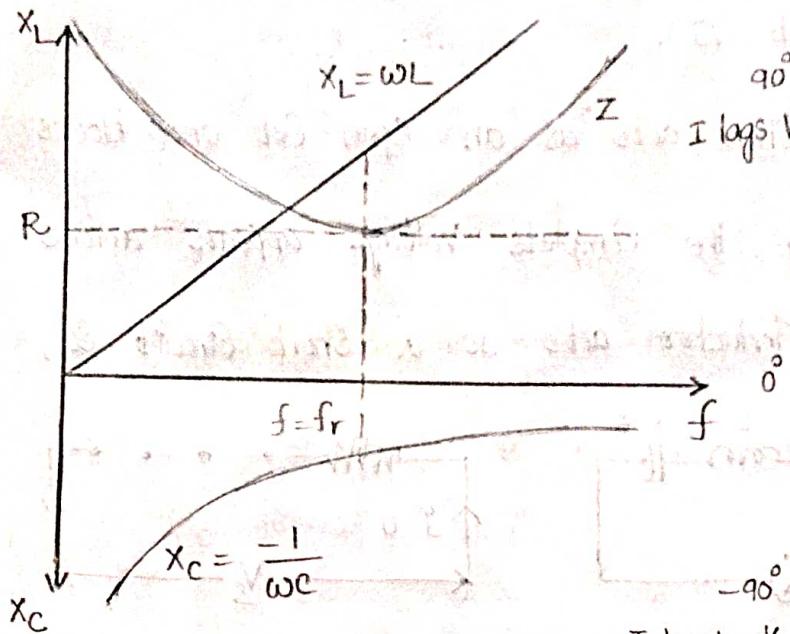


Fig 4.21

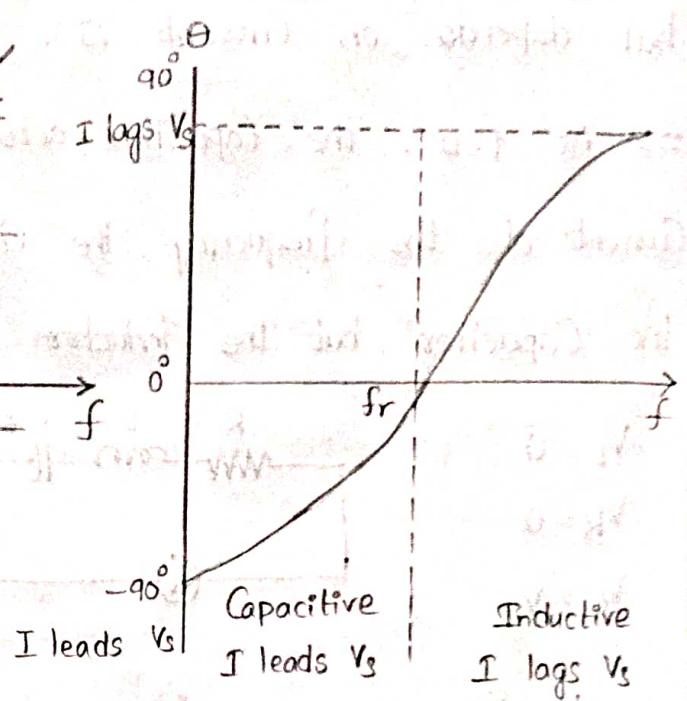


Fig 4.22


### Voltages and Currents in a Series Resonant Circuit:

The Variation of impedance and Current with frequency is

shown in figure.

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$Z = R + j(X_L - X_C)$$

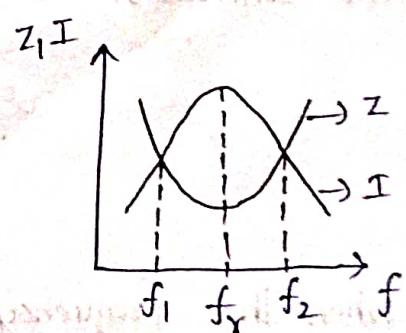

$\Rightarrow$  At resonant frequency, the capacitive reactance is equals to inductive reactance, and hence the impedance is minimum. Because of minimum impedance, Maximum Current flows through the circuit.

The Current Variation with frequency is plotted in figure.

⇒ The Voltage drop across resistance is  $V_R = I \cdot R$

The Voltage drop across Inductance is  $V_L = I \cdot X_L = I \cdot 2\pi f L$

The Voltage drop across Capacitance is  $V_C = I \cdot X_C = I \cdot \frac{1}{2\pi f C}$

From the above drops,  $V_R$  is independent of frequency



but depends on Current (I).

⇒ At  $f=0$ , the Capacitor acts as an Open Circuit and blocks Current at the frequency, the Complete Voltage appears across the Capacitor, but the inductor acts as a short circuit. So,

$$V_L = 0$$

$$V_R = 0$$

$$V_C = V_S$$

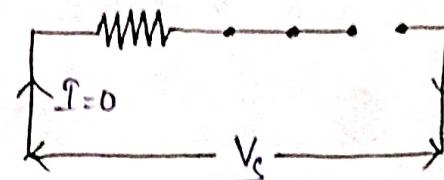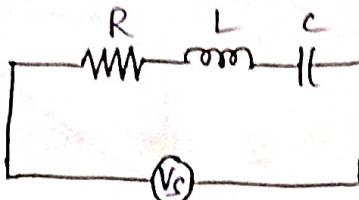

⇒ As the frequency increases,  $X_C$  decreases and  $X_L$  increases, causing total reactance ( $X_C - X_L$ ) to decrease. As a result the impedance decreases and the current increases. As the Circuit Current Increases.

$$V_R \text{ is } \uparrow = I R$$

$$V_L \text{ is } \uparrow = I X_L$$

$$V_C \text{ is } \uparrow = I X_C$$

⇒ when the frequency reaches its resonant value ' $f_r$ ', the impedance is equal to 'R'. i.e.,  $Z = R$ . At this frequency, Current reaches its Maximum Value and  $V_R$  is at Maximum Value.

$$V_R = I R \text{ (Maximum)}$$

$$V_L = V_C \text{ (at resonance)}$$

As the frequency is increased

above resonance,  $X_L$  continues to

(↑) and  $X_C$  continues to (↓),

causing the total reactance


$(X_L - X_C)$  to increase. As a result

there is (↑) in  $z$  and decrease

in current

As frequency becomes very high,

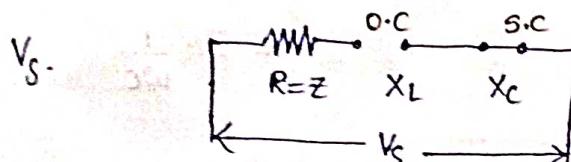$I$  reaches zero, both  $V_R$  and  $V_C$  reaches zero and  $V_L$  reaches



Frequency at which Maximum Value of  $V_L$  Occurs :

The Voltage across an inductor is given by  $V_L = I \cdot \omega L$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = I \cdot \omega L$$

Voltage drop across inductor

$$V_L = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cdot \omega L$$

Squaring on Both Sides

$$V_L^2 = \frac{V^2 \omega^2 L^2}{R^2 + (\omega L - \frac{1}{\omega C})^2} = \frac{V^2 \omega^4 L^2 C^2}{\omega^2 C^2 R^2 + (\omega^2 L C - 1)^2}$$

By differentiating  $V_L^2$  w.r.t  $\omega$  and setting  $\frac{dV_L^2}{d\omega} = 0$ , we get

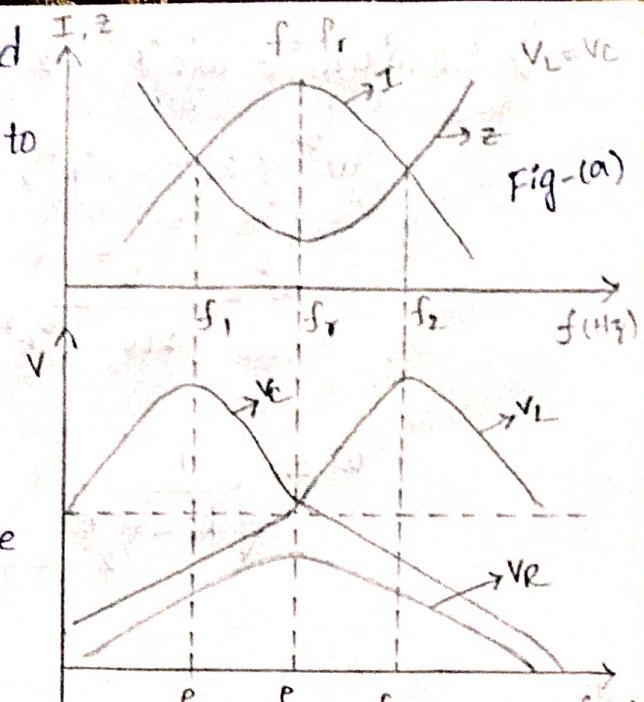


Fig-(b)

$$\Rightarrow 2\omega^2 CL - \omega^2 C^2 R^2 - 2 = 0 \quad \text{at resonance}$$

$$\omega^2 (2LC - C^2 R^2) = 2$$

$$\omega^2 = \frac{2}{2LC - C^2 R^2} = \frac{1}{LC - \frac{C^2 R^2}{2}}$$

$$\omega = \sqrt{\frac{1}{LC - \frac{C^2 R^2}{2}}} \Rightarrow f_L = \frac{1}{2\pi\sqrt{LC - \frac{C^2 R^2}{2}}}$$

Frequency at which Maximum Value of  $V_C$  occurs:

The Voltage across a Capacitor is given by  $V_C = I X_C$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = I \cdot \frac{1}{\omega C}$$

$$V_C = I \cdot X_C = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \cdot \frac{1}{\omega C}$$

Squaring on B.S

$$V_C^2 = \frac{V^2}{\omega^2 C^2 \cdot [R^2 + (\omega L - \frac{1}{\omega C})^2]}$$

$$= \frac{V^2}{\omega^2 C^2 \left[ R^2 + \frac{(\omega^2 LC - 1)^2}{\omega^2 C^2} \right]} = \frac{V^2}{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2}$$

$$= \frac{V^2}{R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2}$$

By differentiating  $V_C^2$  w.r.t to 'w' and Equating to zero

$$\frac{dV_C^2}{dw} = 0 = \frac{-V^2 [2\omega^2 C^2 R^2 + 2(\omega^2 LC - 1) \cdot 2\omega LC]}{[R^2 \omega^2 C^2 + (\omega^2 LC - 1)^2]^2}$$

$$2\omega^2 CR^2 + 2(\omega^2 LC - 1) 2\omega LC = 0$$

$$2\omega^2 C^2 + CR^2 - 2L = 0$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$f_c = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L}}$$

Band width of Series Resonant Circuit:

Here ' $f_1$ ' is called "lower Cut-off frequency" at which Current is 0.707 times the Current of resonant Value, ' $f_2$ ' is called "Upper Cut-off frequency"


Equating ① and ②

$$\frac{1}{\omega_1 C} - \omega_1 L = \omega_2 L - \frac{1}{\omega_2 C}$$

$$L (\omega_1 + \omega_2) = \frac{1}{C} \left[ \frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right]$$

$$\omega_1 \omega_2 = \frac{1}{LC}$$

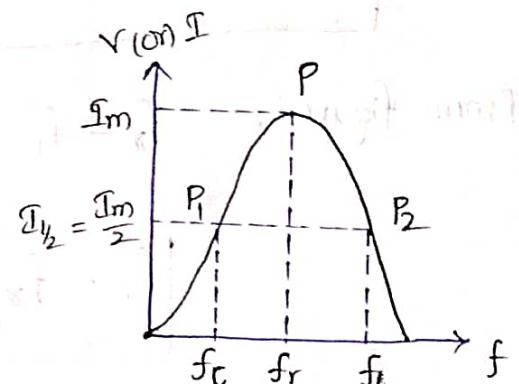We Know,  $\omega_r^2 = \frac{1}{LC}$  So  $\omega_r^2 = \omega_1 \omega_2$



$$\omega_r = \sqrt{\omega_1 \omega_2}$$

$$f_r = \sqrt{f_1 f_2}$$

$\therefore$  The resonant frequency ' $f_r$ ' is the geometric mean of the half-power frequencies  $f_1$  and  $f_2$

By adding ① and ②

$$\frac{1}{w_1 C} + w_1 L + w_2 L - \frac{1}{w_2 C} = 2R$$

$$L(w_2 - w_1) + \frac{1}{C} \left[ \frac{w_2 - w_1}{w_1 w_2} \right] = 2R$$

We Know,  $w_r^2 = \frac{1}{LC}$

$$\Rightarrow C = \frac{1}{L w_r^2}$$

$$(w_2 - w_1) L + \frac{w_r^2 L (w_2 - w_1)}{w_r^2} = 2R$$

$$2L (w_2 - w_1) = 2R$$

$$(w_2 - w_1) = \frac{R}{L}$$

Band width (B.W) =  $f_2 - f_1 = \frac{R}{2\pi L}$

From figure,

$$f_2 - f_1 = \frac{R}{4\pi L}$$

$$f_1 = f_r - \frac{R}{4\pi L}$$

from figure,  $f_2 - f_r = \frac{R}{4\pi L}$

$$f_2 = f_r + \frac{R}{4\pi L}$$

Divide equation ① on B.S with  $f_r$ .

$$f_2 - f_1 = \frac{R}{2\pi L} \Rightarrow \frac{f_2 - f_1}{f_r} = \frac{R}{2\pi f_r \cdot L}$$

$$\frac{f_2 - f_1}{f_r} = \frac{1}{Q} \Rightarrow \frac{BW}{f_r} = \frac{1}{Q}$$

$$Q = \frac{fr}{B \cdot w} \quad (\text{or})$$

$$Q = \frac{fr}{f - f_1}$$

Quality factor: It is Ratio of Reactance to resistance

$$Q = \frac{x}{R} = \frac{x_L}{R} = \frac{x_C}{R} \quad [\text{OR}]$$

Quality factor is defined as ratio of  $\frac{\text{Reactive power}}{\text{Active power}}$

$$Q = \frac{\text{Reactive power}}{\text{Resistive (or) Active power}} = \frac{X^2}{P^2 R} = \frac{X}{R}$$

$$Q = 2\pi \times \frac{\text{Maximum Energy stored}}{\text{Energy dissipated Per Cycle}}$$

For Inductor: Maximum Energy stored =  $\frac{1}{2} L I_m^2$

$$\begin{aligned} \text{Energy dissipated per cycle} &= \frac{I^2 R}{f} = \frac{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times R}{f} \\ &= \frac{\frac{I_m^2}{2} \times R}{f} \end{aligned}$$

$$\therefore Q = 2\pi \times \frac{\frac{1}{2} \times L I_m^2 \times f}{\frac{I_m^2}{2} \times R} = \frac{2\pi L f}{R}$$

$$Q = \frac{2\pi f L}{R} = \frac{\omega L}{R} = \frac{x_L}{R}$$

For Capacitor: Maximum Energy stored =  $\frac{1}{2} C V_m^2$

$$= \frac{1}{2} C \left(\frac{I_m}{\omega C}\right)^2$$

$$= \frac{1}{2} \cdot C \cdot \frac{I_m^2}{\omega^2 C^2}$$


$$\text{Energy dissipated per cycle} = \frac{I^2 R}{f} = \frac{\frac{I_m}{\sqrt{2}} \cdot R}{f}$$

$$= \left(\frac{I_m}{\sqrt{2}}\right)^2 \times \frac{R}{f} = \frac{I_m^2}{2} \cdot \frac{R}{f}$$

$$Q = 2\pi \times \frac{1}{2} \cdot \frac{\omega I_m^2}{w^2 C} = \frac{2\pi f \times \frac{1}{w^2 C}}{R}$$

$$Q = \frac{1}{wC} = \frac{X_C}{R}$$

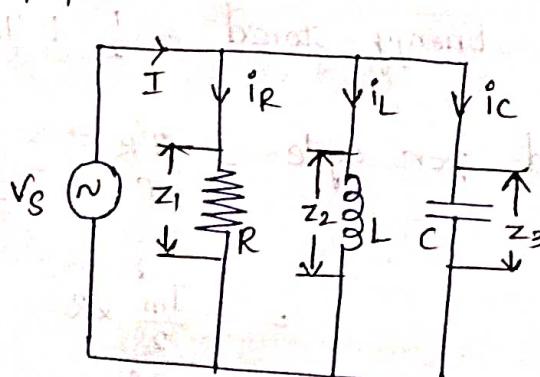Parallel Resonance: Consider a parallel connection of ideal elements  $R, L, C$ .



Parallel Resonance (or) Anti Resonance is a condition in parallel Ckt in which the effect of inductive and capacitive reactance (Susceptance) completely neutralize, The impedance increases to maximum value [ $Z=R$ ] and the current falls to minimum value ( $I=\frac{V}{R}$ ) with a unity power factor.

If we vary supply frequency at particular frequency Net Susceptance of the circuit equals to zero. The frequency at which this condition occurs is known as Resonant

frequency.

$$Y = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C}$$

$$Y = \frac{1}{R} + j \left( \frac{1}{X_C} - \frac{1}{X_L} \right)$$

$$Y = G + j(B_C - B_L)$$

where  $G$  is Conductance

$B_C$  is Capacitive Susceptance

$$\omega_C = 2\pi f_C$$

$B_L$  is inductive Susceptance  $\frac{1}{\omega_L} = \frac{1}{2\pi f_L}$

At resonance  $B_C = B_L$  i.e.,  $B_C - B_L = 0$

$$\frac{1}{X_C} - \frac{1}{X_L} = 0$$

$$\frac{1}{X_C} = \frac{1}{X_L}$$

$$\omega_C = \frac{1}{\omega_L}$$

$$\omega^2 = \frac{1}{LC}$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$f = f_r = \frac{1}{2\pi\sqrt{LC}}$$

Variation of Capacitive and Inductive Susceptance, Impedance.

and Current with frequency :

$$Y = G + jB = G + j(B_C - B_L)$$

$$= \frac{1}{R} + j \left( \frac{1}{X_C} - \frac{1}{X_L} \right)$$

$$= \frac{1}{R} + j \left( \omega_c - \frac{1}{\omega_L} \right)$$

$$= \frac{1}{R} + j \left( 2\pi f_C - \frac{1}{2\pi f_L} \right)$$

(ii) At  $f=0$ ,  $\gamma = \infty$ ,  $z=0$  and  $I \uparrow$

$$f = \infty, \quad Y = 0, \quad z = \infty \quad (\text{and } I \downarrow)$$

$$f = f_r, \quad Y = G, \quad Z = \frac{1}{G} = R \quad \text{and} \quad I^{\min}$$

$$(ii) B_L = \frac{1}{x_L} = \frac{1}{\omega_L} = \frac{1}{2\pi f_L}$$

$$B_L \propto \frac{1}{f}$$

$$(iii) B_c = \frac{1}{x_c} = \omega_c = 2\pi f_c$$

$$B_C \propto f$$

(iv)  $G_1$  is independent of  $f_{B_L}$

$$I = I_L \cdot \cos \phi_f$$

$$I_L = \frac{V}{Z_L}$$



$$\cos \phi_L = \frac{R}{z}$$

$$I = \frac{V}{Z_L} \cdot \frac{R}{Z_L} = \frac{VR}{Z_L^2} = \frac{VR}{L/C}$$

$$= \frac{V_{I,L}}{R_C}$$

$$I = \frac{V}{Z}$$

$$\therefore Z_L = \frac{L}{C}$$

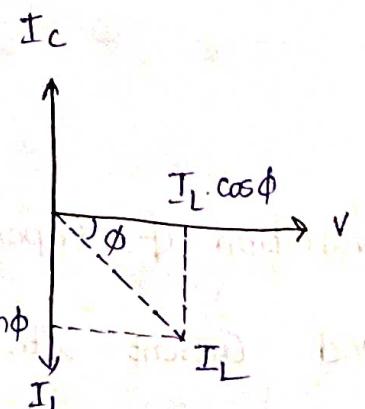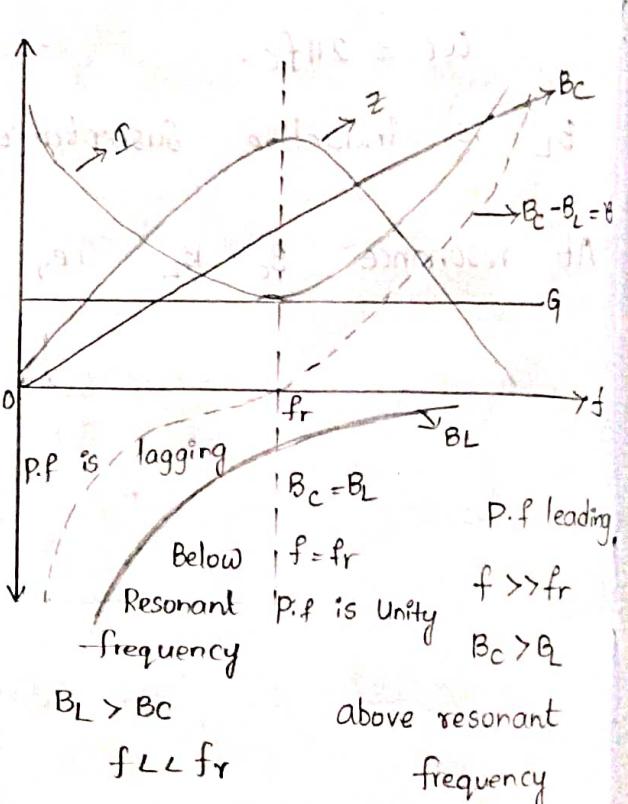


# Band width (BW) of parallel Resonant Circuit:

So, Band width is given by

$$\therefore \text{BW} = f_2 - f_1$$

where,  $f_1$  = lower Cut-off frequency

$f_2$  = higher Cut-off frequency

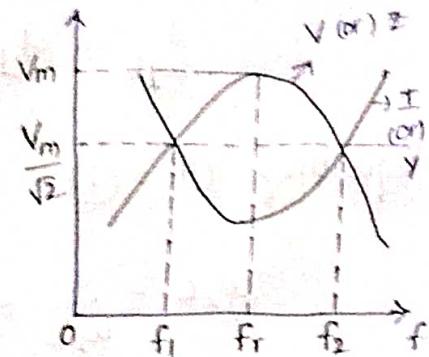

So, Power  $P = \frac{V_m^2}{R} = V_m^2 G \rightarrow ①$

at  $P_1 = \left(\frac{V_m}{\sqrt{2}}\right)^2 * G = 0.5 P$

$P_2 = 0.5 P$

Now, power delivered to the resistance at the  $f_1$  and  $f_2$  is equal to 0.5 times of power at Resonance frequency.

$\therefore$  Power of half power frequencies of  $f_1$  &  $f_2 = 0.5 V_m^2 G$

$$(V_m^2 G)_{f_2} = 0.5 V_m^2 G$$

$$\left(\frac{I}{Y}\right)^2 G = \frac{1}{2} \left(\frac{I}{G}\right)^2 \times G$$

$$\left(\frac{1}{\sqrt{G^2 + (B_C - B_L)^2}}\right)^2 = \frac{1}{2G^2} \Rightarrow \frac{1}{G^2 + (B_C - B_L)^2} = \frac{1}{2G^2}$$

$$(B_C - B_L)^2 = G^2 \Rightarrow B_C - B_L = \pm G \quad (B_C - B_L)^2 = 2G^2 - G^2$$

$$(B_C - B_L)^2 = G^2$$

At  $f_2 \quad B_C - B_L = G \rightarrow ②$

$$B_C - B_L = \pm G$$

$$\omega_2 C - \frac{1}{\omega_2 L} = Y_R \rightarrow ③$$

$f_1$  (lower-cut off frequency),  $B_C - B_L = -G$

$$(or) \quad B_L + B_C = G_1 \quad \rightarrow (2)$$

$$\frac{1}{\omega_1 L} - \omega_1 C = \frac{1}{R} \rightarrow (3)$$

Equating (1) = (2)

$$\omega_2 C - \frac{1}{\omega_2 L} = \frac{1}{\omega_1 L} - \omega_1 C$$

$$C [ \omega_2 + \omega_1 ] = \frac{1}{L} \left[ \frac{\omega_2 + \omega_1}{\omega_1 \omega_2} \right]$$

$$\omega_r \omega_2 = \frac{1}{L C} \rightarrow (4)$$

$$\text{We Know, } \omega_r^2 = \frac{1}{LC}$$

Compare with equation (4)

$$\omega_r \omega_2 = \omega_r^2 = \omega_r = \sqrt{\omega_1 \omega_2}$$

$$f_r = \sqrt{f_1 f_2}$$

$$\text{Adding (1) + (2), } \frac{1}{\omega_1 L} - \omega_1 C + \omega_2 C = - \frac{1}{\omega_2 L} = \frac{1}{R} + \frac{1}{R}$$

$$C [ \omega_2 - \omega_1 ] + \frac{1}{L} \left[ \frac{1}{\omega_1} - \frac{1}{\omega_2} \right] = \frac{2}{R}$$

$$C [ \omega_2 - \omega_1 ] + \frac{1}{L} \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] = \frac{2}{R}$$

$$C [ \omega_2 - \omega_1 ] + C \omega_r \cdot \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] = \frac{2}{R}$$

$$2C [ \omega_2 - \omega_1 ] = \frac{2}{R}$$

$$\omega_2 - \omega_1 = \frac{1}{RC}$$

$$f_2 - f_1 = \frac{1}{2\pi RC}$$

so, we know that,

$$Q = \frac{f_r}{B.W} = \frac{1}{2\pi\sqrt{LC}} \times 2\pi RC$$

$$Q = R \cdot \sqrt{\frac{C}{L}}$$

Quality factor for parallel Resonant Circuit:

$$Q = 2\pi \left[ \frac{\text{Energy stored in Inductor}}{\text{Energy dissipated per cycle}} \right]$$

For Inductor:

$$= 2\pi \left[ \frac{\frac{1}{2} L I^2}{\frac{I^2}{R} \times R \times \frac{1}{f}} \right] \quad \text{where } I = \frac{V}{\omega L}$$

$$I = \frac{V}{R}$$

$$= 2\pi \left[ \frac{L \left( \frac{V}{\omega L} \right)^2}{\left( \frac{V}{R} \right)^2 \cdot R \cdot \frac{1}{f}} \right] = 2\pi \left[ \frac{1}{(2\pi f L)} \times R \times f \right]$$

$$= \frac{R}{2\pi f L}$$

$$Q = \frac{R}{2\pi f L} = \frac{R}{X_L}$$

For Capacitor:

$$Q = 2\pi \left[ \frac{\frac{1}{2} C V_m^2}{\frac{V_{rms}^2}{R} \cdot \tau} \right] = \pi \left[ \frac{C \cdot V_m^2}{\left( \frac{V_m}{V_r} \right)^2 \cdot \frac{1}{R} \cdot \tau} \right]$$

$$= 2\pi \left[ \frac{C \cdot R}{\tau} \right]$$

$$= 2\pi f \cdot C \cdot R = \omega_c \cdot R$$

$$Q = \frac{R}{X_C}$$